

The new standard components!

Using Cheap Asian Electronic Modules Part 1

This is the first of a series of small articles which will help you take advantage of the wide range of handy pre-built electronic modules that are now available from Asia. This month, we review the DS3231 real-time clock (RTC), which is the perfect partner for popular microcontrollers like the Arduino or Micromite.

IF YOU'VE been reading *EPE* for a while now, you'll have noticed that small electronic modules have been creeping into our projects.

These are not just Micromite, Arduino or Raspberry Pi boards, but really small and low-cost modules including real-time clocks/calendars (RTC), USB-to-UART serial 'bridges', UHF data transmitters and receivers, DDS signal generators, OLED/LCD panels, touch-screen TFT LCDs, temperature/humidity sensors, microSD card interfaces and many more. They seem to be breeding like rabbits!

Many of these modules have sprung into life initially as 'peripherals' for baby micros like the Arduino (ie, shields) and Raspberry Pi. But most of them have a lot of other applications in circuits and designs using standard TTL or CMOS ICs, and even in designs using olde-worldle discrete transistors.

But the really big advantage of this new generation of pre-built modules is that most of them are surprisingly low in cost. In fact, with many of them, you'll find that the cost of a complete module is much less than the price you'd pay for the main IC chip used in them.

A prime example is the popular real-time clock/calendar module using Maxim's very accurate DS3231 RTC chip — plus a 24C32 4KB EEPROM, in most cases. Although the module is usually advertised as intended to be used with an Arduino, it has a standard I²C ('Inter-IC') in-

terface and can actually be used with most other micros (we used it with the Micromite in our *Touchscreen Super Clock*).

So that's the rationale behind this series of articles on the new 'el cheapo' modules. They're readily available, often have many applications and they're usually much cheaper than building up the same circuits for yourself. As a result, they've now reached the status of being just standard circuit components. The Electronic Modules As Components or 'EMAC' revolution has begun!

Let's get the ball rolling by looking at real-time clock/calendar modules.

RTC modules

Probably the first low-cost RTC modules to appear were those based on the Philips/NXP PCF8563 chip, a low-power 8-pin CMOS device which has an I²C interface but needs an external 32.768kHz crystal. Modules based on the PCF8563 are still available at low cost from eBay or AliExpress, but they tend to be less popular than

modules based on one of two newer Maxim chips: either the DS1307 or the DS3231.

Like the PCF8563, the DS1307 needs an external 32kHz crystal. However, it also has a built-in power sense circuit which switches to a backup battery when it detects a power failure. It has 56 bytes of internal non-volatile SRAM and a standard I²C interface, making it compatible with just about every type of microcontroller module such as the Arduino or the Micromite.


It does have one shortcoming, though: the time-keeping accuracy is inclined to drift a little with temperature and so it can vary by a few minutes a month.

Clock/calendar modules using the DS1307 tend to cost more than those using the PCF8563, but they often include extras like a DS18B20 temperature sensor and a 24C32 serial EEPROM (32Kbits = 4KB). This makes them quite attractive for applications where extreme accuracy isn't too critical.

But modules based on the DS3231 chip are currently the most popular, partly because the DS3231 has an on-chip temperature-compensated crystal oscillator and crystal.

It also includes an internal temperature-compensated voltage reference and comparator, both to maintain its own supply voltage and to automatically switch to a backup supply when necessary.

 These features allow it to provide significantly higher timekeeping accuracy: better than ± 2 ppm between 0



Top view of the DS3231 module

and 40°C, or ±2 minutes per year for a temperature range of -40°C to +85°C. Its single shortcoming compared with the DS1307 is that it lacks the internal non-volatile SRAM.

Despite the advantages offered by the DS3231, modules using it tend to cost no more than those based on the DS1307 or the PCF8563. And this applies for modules like the one shown in the pictures, which also includes a 24C32 serial EEPROM.

As mentioned earlier, this is the RTC module that has been used in a number of recent projects like the *Touchscreen Super Clock* and the *Micromite Explore 100*, so it's the one we'll now concentrate on.

DS3231 RTC

As shown in the circuit diagram of Fig.1, there isn't a great deal in this module apart from the DS3231 chip itself (IC1), its 3.6V backup battery and the 24C32 serial EEPROM (IC2). We'll discuss the rest of the components and circuitry shortly after we've looked at what's inside the DS3231.


Its compact 16-pin small outline (SO) SMD package contains an I²C data bus interface, address decoding for the 18 internal time, date and control registers, a temperature sensor and a power control circuit which can swing over to the backup battery when the supply voltage (V_{CC}) fails. Its block diagram is shown in Fig.2.

Then there's a complete temperature-compensated 32.768kHz crystal oscillator (TCXO), followed by a frequency divider chain and all of the time (seconds/minutes/hours), date (day of week, day of month, month and year), alarm, status and control registers. Finally, there's reset circuitry plus output buffers for both the 32kHz TCXO oscillator and the square wave output when it's enabled.

Note that since the module tracks the date as well as the time, it is more correctly described as a real-time clock and calendar (RTCC) module but we'll stick with the more common RTC term.

As well as the time and date registers, the DS3231 also provides two time-of-day alarm functions which are programmable via two sets of dedicated registers. These can generate an interrupt output signal via pin 3 (INT/SQW), for feeding directly back to a micro.

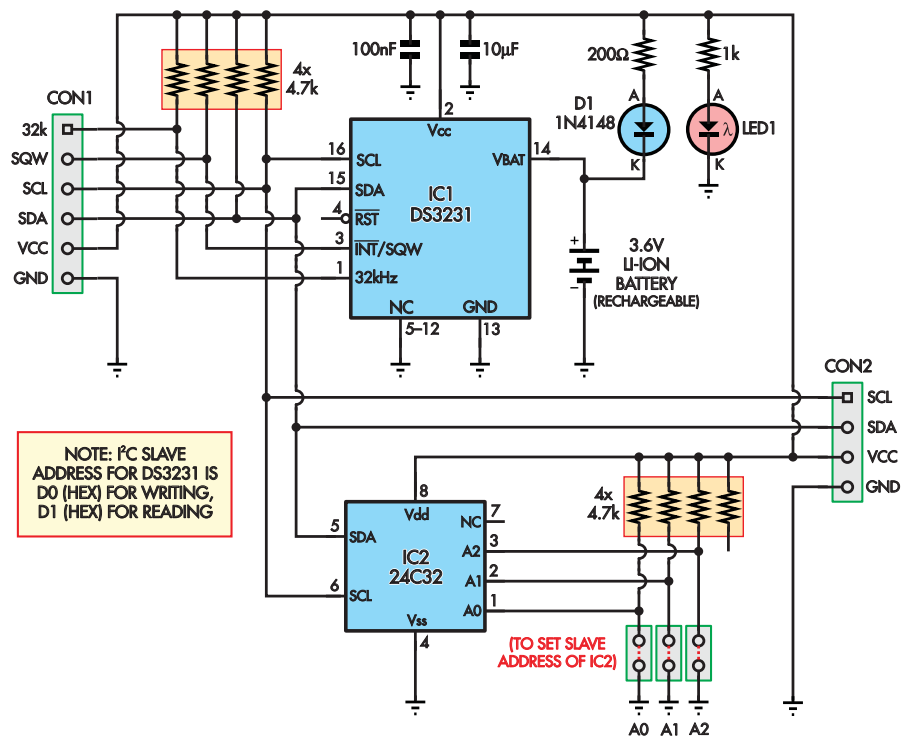When pin 3 is not being used to provide this alarm interrupt function, it can be used to provide square wave timing signals derived from the 32kHz TCXO. The square waves can be programmed for one of four frequencies: 1Hz, 1.024kHz, 4.096kHz or 8.192kHz.



NOTE: I²C SLAVE ADDRESS FOR DS3231 IS D0 (HEX) FOR WRITING, D1 (HEX) FOR READING

I ² C SLAVE ADDRESSES (HEX) FOR 24C32 EEPROM					
MSD (FIXED)	A2	A1	A0	WRITE	READ
A	1	1	1	AE	AF
A	1	1	0	AC	AD
A	1	0	1	AA	AB
A	1	0	0	A8	A9
A	0	1	1	A6	A7
A	0	1	0	A4	A5
A	0	0	1	A2	A3
A	0	0	0	A0	A1

← DEFAULT ADDRESS (NO LINKS ON PADS FOR A0, A1 OR A2)

 


Fig.1: complete circuit for the DS3231-based RTC module. Both CON1 and CON2 provide serial bus and power connections, allowing extra devices to be connected. Note that the I²C bus should have only one set of pull-up resistors.

These are in addition to the 32.768kHz signal made available at pin 1.

All of the DS3231's function settings, along with the initial time and date, can be programmed using the I²C bus to write into the appropriate internal registers. Then the time, date and status can be subsequently obtained by using the I²C bus to read from the same registers.

Pins 15 and 16 of the device are used for the I²C bus connections: pin 15 for the SDA serial data line and pin 16 for the SCL serial clock line. On the module shown, these are both provided with surface-mount 4.7kΩ pull-up resistors to V_{CC}, as are pin 1, the 32.768kHz output and pin 3, the INT/squarewave output. (The latter two pins are open-drain outputs, so they need the external pull-up resistors.)

That's probably about all you need to know about the DS3231 itself, apart from the way that pin 14 (V_{BAT}) is used for the connection to the 3.6V lithium-ion rechargeable backup battery. In the module shown here, diode D1 and its series 200Ω resistor are used to maintain the battery charge when V_{CC} is

connected to the module. LED1 and its series 1kΩ resistor are used to provide a power-on indicator. We'll have more to say about battery options later.

Note the two I/O headers, labelled in Fig.1 as CON1 and CON2. CON1 provides pins for both the 32kHz and SQW/INT outputs, as well as the SCL/SDA/V_{CC}/GND bus connections, while CON2 provides only the latter four connections, essentially to allow daisy-chaining further devices to the I²C bus – additional memory chips, for example.

Now let's look at IC2, the 24C32 serial EEPROM chip, which is something of a bonus. The 24C32 is a 4KB (32Kb) device, with a standard I²C serial interface. In this module, the SDA line (pin 5) and SCL line (pin 6) are connected in parallel with those for IC1, to the module's SDA and SCL lines at both CON1 and CON2.

To allow IC2 to be addressed by the micro without conflicting with commands or data sent to or received from IC1, it has a different slave address on the I²C bus. In fact, it can have any of eight different slave

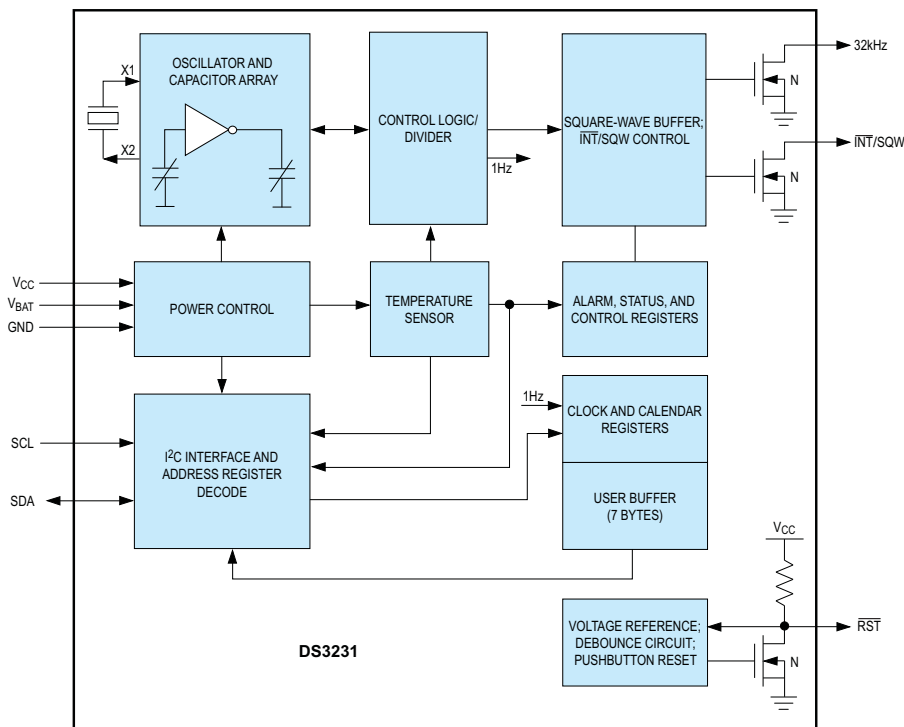


Fig.2: block diagram for the DS3231. A comparator monitors both V_{CC} and V_{BAT} and the DS3231 is powered from whichever is higher. The oscillator is automatically temperature-compensated for accuracy.

addresses, as set by the voltage levels of pins 1, 2 and 3 (labelled A0, A1 and A2).

As shown in Fig.1, the module pulls all three pins up to V_{CC} via the 4.7k Ω resistors by default, which gives IC2 a slave address of AE/AF hex (AEh for writing, AFh for reading). But it also provides three pairs of pads on the PCB so that any of the three address pins can be pulled low (to ground) by soldering across the A0, A1 or A2 pads. This allows the slave address of IC2 to be set to any of the eight possible values, as shown.

So since the slave address of IC1 (the DS3231) is fixed at D0/1 hex (D0 for writing, D1 for reading), there is no conflict. In fact, the main reason for changing the slave address of IC2 via the wire links would be to avoid a conflict with any other devices that may be attached to the I²C bus.

How it's used

Since both the DS3231 and 24C32 devices on the module are intended for

use via the I²C bus, this makes it easy to use with any micro or other system provided with at least one I²C interface. (Even if you don't have such an interface, you can use two GPIO pins in 'bit banging' mode, but that's outside the scope of this article.)

For example, to use it with an Arduino Uno or similar all you need to do is connect the SCL line on the module to the AD5/SCL pin on the Arduino, the SDA line to the AD4/SDA pin, the V_{CC} pin to the +5V pin and the GND pin to one of the Arduino's GND pins.

It's just as easy with the Micromite. In this case, the SCL pin connects to pin 17 on the Micromite's main I/O pin strip, while the SDA pin connects to pin 18 next to it. Then the V_{CC} and GND pins connect to the +5V pin and GND pins on the same pin strip.

Programming either of the chips on the module should also be fairly straightforward, because of the I²C interfacing. The main thing to remember is that I²C transactions always begin with a control byte sent by the master (the microcontroller), specifying the address of the slave device it wishes to communicate with and whether it wants to write to or read from the device.

So, for example, the control byte to initiate a write

operation to one of the registers in the DS3231 would be D0h, while the control byte to read from one of the addresses in the 24C32 would be AFh (assuming it's at the default address on your module).

After the slave device sends back an 'ACK' or acknowledge indication (to show that it's present and ready for a transaction), the micro then sends the address of the register or memory location in the device that it wants to write data to or read it from. When this has been acknowledged, the actual write or read transactions can take place.

If this sounds a bit complicated, you'll be relieved to hear that if you're using one of the popular micros like the Arduino or Micromite, you probably don't need to worry about this yourself. That's because this has usually been taken care of in small code libraries, with functions specifically written for I²C data communications.

In the case of the Micromite, in fact, I²C communication is handled by the MMBASIC interpreter.

For example, if you are using an Arduino, the Arduino IDE application already includes a 'Wire' library, providing about nine different functions for passing data between the micro and an I²C device.


Similarly, if you're using a Micromite, you'll find that Geoff Graham's MMBASIC already includes functions like RTC SETTIME, RTC GETTIME, RTC SETREG and RTC GETREG specifically for talking to the DS1307 or DS3231 RTC devices. And there are other functions like I2C OPEN, I2C WRITE, I2C READ and I2C CLOSE for data transactions with other I²C devices (like the 24C32 EEPROM chip in the current module).

Finally, there's also an automatic variable called MM.I2C, which can be read after any I²C transaction to find out the result status.

So all in all, the RTC module shown with its DS3231 clock/calendar chip (and bonus 24C32 EEPROM chip) is relatively easy to use, and exceptional value for money.

Here is a link to a useful web tutorial by John Boxall of tronixlabs, explaining how to use either the DS1307 or DS3231 RTC modules with an Arduino: <http://bit.ly/2yTbIWy>

 Final note: this module has onboard pull-up resistors for the I²C bus, you may need to remove them, or avoid fitting pull-up resistors on the master, for it to share a bus with other peripherals.




Rear view of the DS3231 module showing the 3.6V Li-ion backup battery (pin 14) which powers the real time clock when the supply voltage (V_{CC}) fails.

Reproduced by arrangement with SILICON CHIP magazine 2017. www.siliconchip.com.au



DS3231 High Precision Real Time Clock

 DS3231 is a low cost and extremely accurate I2C real-time clock, with an integrated crystal and temperature-compensated crystal oscillator (TCXO). DS3231 can be operated using supply voltages ranging from 2.3V to 5.5V and it also features battery backup capabilities. The on-board AT24C32 32KB EEPROM that can be used to add non-volatile data storage to your electronic projects and prototypes.



SKU: [MDU-1036](#)


Brief Data:

- Standard 2.54mm pins pitch for input and output connections.
- Two programmable square-wave outputs.
- Backup battery socket compatible with CR2032 3V Lithium batteries.
- Clock accuracy: ± 2 ppm.
- 32KB EEPROM Memory chip: AT24C32.
- On-chip temperature sensor with an accuracy of $\pm 3^{\circ}\text{C}$.
- I2C bus interface maximum speed: 400kHz.
- Small Size: 38 x 22 x 14 mm.

Using Cheap Asian

Electronic Modules Part 2

 The HC-SR04 Ultrasonic Distance Sensor Module



In the second article on cheap pre-built electronics modules, we're focusing on the HC-SR04 ultrasonic distance sensor module. We describe how the module works and show how it can be used as a hallway monitor or door sentry.

IF THE HC-SR04 module shown in the picture looks familiar, that's because it has already been used in Geoff Graham's *Ultrasonic Garage Parking Assistant*, published in the June 2017 issue. But this module doesn't have to be used with a microprocessor module like a Micromite or an Arduino, it can also be used with much simpler circuitry.

Before we get to how it works, we should note that these ultrasonic sensor modules have been around for about six years, beginning life as an add-on 'shield' for the Arduino. Since then, they have gone through a number of iterations, all bearing the same HC-SR04 label but with various minor circuit and component changes. We suspect this has been due to various manufacturers working out ways of

By **JIM ROWE**

reducing costs, rather than seeking to achieve better performance.

The bottom line is that although some of these slightly different HC-SR04 modules are still being sold, they all seem to function and perform much the same. So don't worry if the module you buy looks a little different from that shown in the photos. The odds are that if your module carries the label HC-SR04, it will work just like any other HC-SR04.

Current HC-SR04 modules are based on a PCB measuring 45 × 20mm. On the top side of the PCB is a pair of small (16mm diameter) ultrasonic transducers with a 4MHz crystal between them.

All the components on the other side of the PCB are surface-mount types, apart from the 4-pin right-angle header at bottom centre. Fig.1 shows how it's used. It sends out a burst of ultrasonic energy from the transmitter transducer (the one marked T, on the left) and then listens via the other receiver transducer (marked R, on the right) for any echo that may be reflected back from an object in front of the module (see Fig.1).

If it detects this ultrasonic echo, it produces an output pulse with a width approximately proportional to the distance between the module's sensors and the object producing the echo.

The ultrasonic frequency used is very close to 40kHz, roughly double

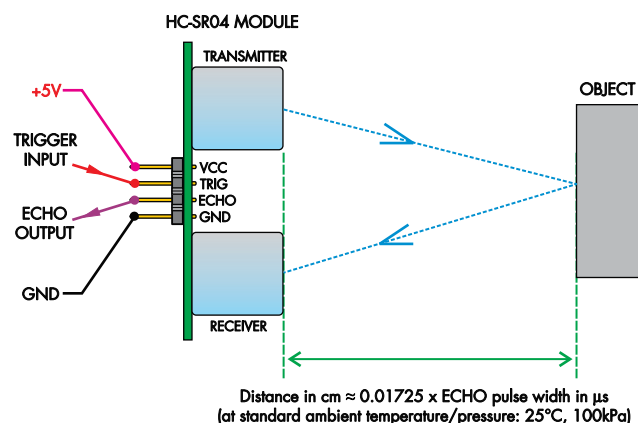


Fig.1: one ultrasonic burst is sent out from the transmitter transducer. The receiver transducer will detect this burst if it is reflected off an object in front of the module. Once detected by the receiver, an output pulse is produced with a width in microseconds of (distance in cm) ÷ 0.01725.

 


Fig.2: there must be a delay of 60ms between trigger pulses to prevent late echoes from affecting successive readings.

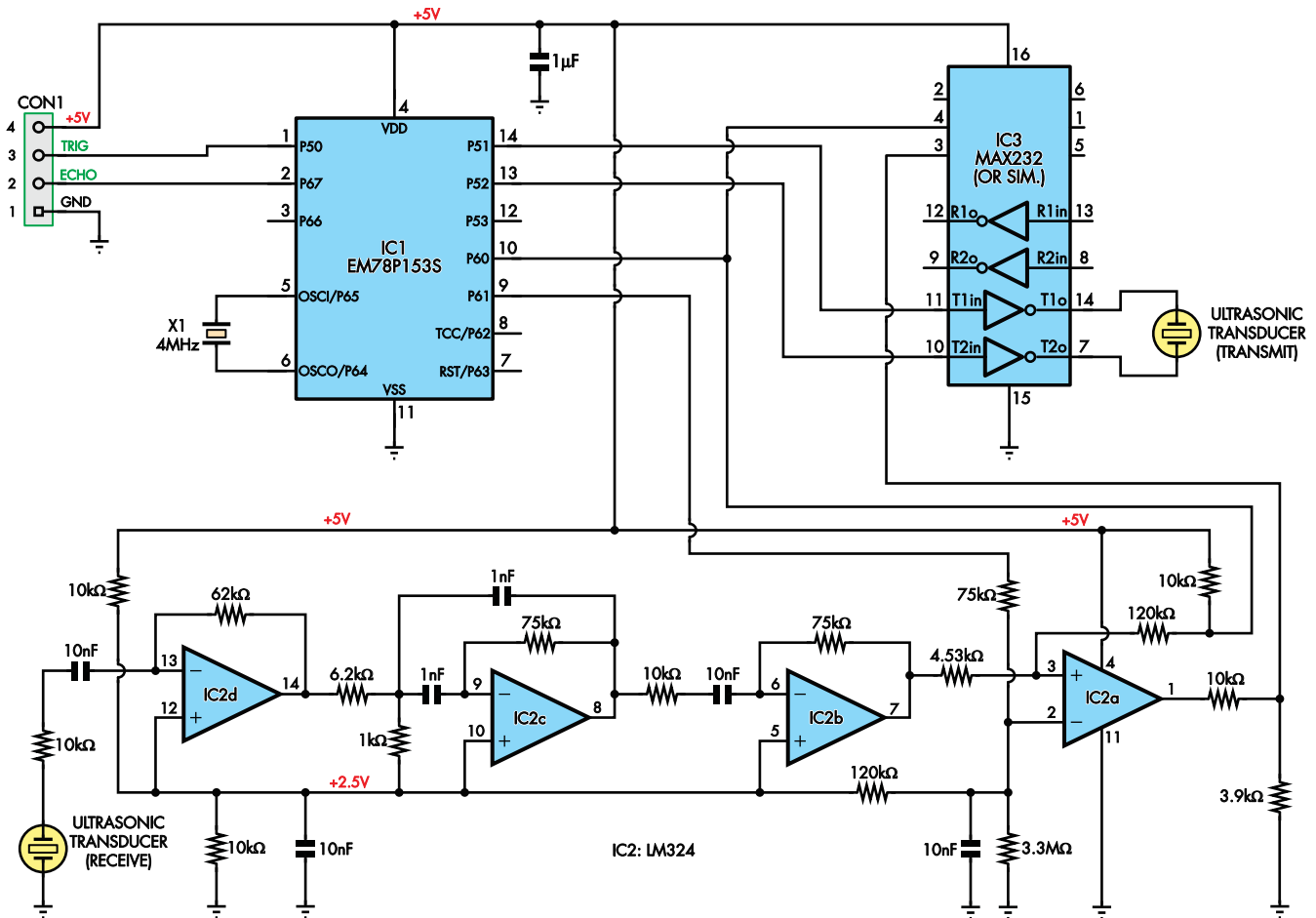


Fig.3: complete circuit diagram for the HC-SR04 ultrasonic sensor module. When IC1 detects a TRIG pulse at pin 1, a 40kHz burst signal of eight pulses is generated at pins 10 and 14 of IC1. This is taken to pins 10 and 11 of IC3 respectively, and output at pins 7 and 14 connecting to the transmit transducer.

the highest frequency that can be heard by human ears. The burst of transmitted energy consists of eight pulses at 40kHz, so the transmitted burst lasts for only 200µs, as shown in Fig.2.

Since the speed of sound in air at 25°C and 100kPa (ie, 1 bar) is close to 345m/s (= 0.0345cm/µs) and the distance travelled by the ultrasonic burst energy corresponds to double the distance between the transducers and the reflecting object, we can calculate the distance from the delay as follows:

$$\begin{aligned} \text{distance in cm} &= \\ &= \frac{0.0345 \times \text{echo pulse width } (\mu\text{s})}{2} \\ &= 0.01725 \times \text{echo pulse width } (\mu\text{s}) \end{aligned}$$

As shown in Fig.2, each measurement cycle begins when a positive trigger pulse of at least 10µs duration is applied to the HC-SR04 module's trigger input pin. When the echo has been detected, it then produces a pulse at the echo output pin. Note that there should be at least 60ms between trigger pulses, to prevent late echoes from one cycle causing false readings on the next. So in practice, it's a good idea to limit the trigger pulse frequency to no more than 16Hz.

Circuit details

The full circuit for the HC-SR04 module is shown in Fig.3. It is based on an EM78P153S microcontroller (IC1), a low-power 8-bit CMOS device made by Elan Microelectronics in Hsinchu, Taiwan. This device has a 1024 × 13 bits one-time programmable (OTP) ROM plus 32 bytes of on-chip SRAM, and comes in a 14-pin SOIC package. It runs here with a 4MHz crystal between pins 5 and 6.

When a TRIG pulse arrives at pin 1 of IC1 (from pin 3 of CON1), the controller generates a 40kHz burst signal of eight pulses at pins 13 and 14, with one pin 180° out of phase with the other. These go to pins 10 and 11 of IC3, a bus driver IC very similar to the MAX232. The outputs from IC3 (pins 7 and 14) connect across the transmitter transducer, effectively driving it in bridge mode to emit the bursts of ultrasonic energy.

Echoes picked up by the receive transducer pass through the four sections of IC2, an LM324 quad op amp. These provide amplification, band-pass filtering and phase detection, with the result that a received echo pulse is fed back to pin 10 of IC1. The micro then compares the timing of the leading edge of this received

echo pulse with the leading edge of the transmitted burst fed to IC3 and the transmit transducer, and produces an echo output pulse at pin 2 with its width equal to the time difference. This echo output pulse appears at pin 2 of CON1.

How it's used

If you want to use the HC-SR04 module to actually measure the distance to an object or wall in front of it, the best way to do it is to hook it up to a microprocessor module like an Arduino, Micromite or Raspberry Pi. The micro's program generates the trigger pulse to the HC-SR04, then measures the length of the echo pulse and calculates the corresponding distance.

There's no need to worry about writing a program to do these tasks for you, because many people have already produced programs to do this. A quick search on the Arduino website (www.arduino.cc) or by using Google will find a sample program for the micro you're using in short order.

If you want to use the HC-SR04 with a Micromite, Geoff Graham has already built a DISTANCE function into his MMBasic programming language for the Micromite family to make it really easy.

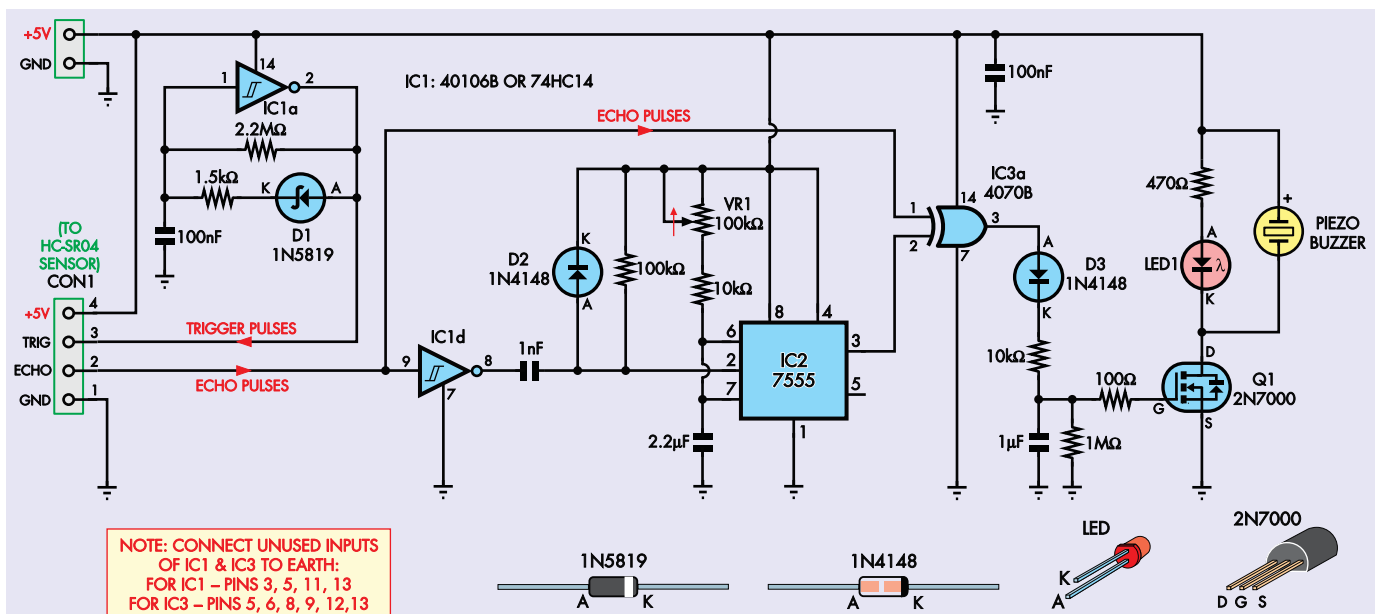


Fig.4: complete circuit for an ultrasonic intruder alarm using an HC-SR04 module. IC1a generates 60μs-wide trigger pulses at 12Hz, which are fed to pin 3 of CON1. The echo pulses trigger monostable multivibrator IC2, and IC3a then compares the width of the resulting pulse to the echo pulse. If these differ, LED1 lights and the piezo buzzer sounds.

All you have to do to get the Micromite to trigger the HC-SR04 and then calculate the object distance from the echo pulse is use this one-line function call:

$$d = \text{DISTANCE}(\text{trig}, \text{echo})$$

Where 'd' is the distance in centimetres, 'trig' is the Micromite's I/O pin connected to the HC-SR04's trigger input pin and 'echo' is the I/O pin connected to the HC-SR04's echo output pin.

The only extra step is to connect the HC-SR04's +5V and GND pins to the corresponding pins of your Micromite.

If you want to display the result 'd' on an alphanumeric LCD, you can do this using commands like:

```
LCD INIT ...
LCD 1, 2, "Distance = "
LCD 2, 6, STR$(d)
and so on.
```

You can get a good idea of what's involved in using the HC-SR04 with a Micromite from Geoff Graham's article describing the *Ultrasonic Garage Parking Assistant*.

But say you want to use this module without a microcontroller at all. That's fairly straightforward, as we'll now demonstrate.

A simple intruder alarm

For example, to use it as an ultrasonic intruder alarm, have a look at the circuit shown in Fig.4. It uses three low-cost CMOS ICs, a 2N7000 MOSFET, three diodes, one LED, a piezo buzzer and some passive components.

This circuit and the HC-SR04 operate from a common 5V DC power supply, which can be from a USB plugpack or USB power bank.

IC1 is a hex Schmitt trigger inverter package and we're using just two sections of it, IC1a and IC1b. IC1a at upper left is connected as a relaxation oscillator, to generate a stream of 60μs-wide pulses at a frequency of about 12Hz, ie, with a pulse spacing of about 83ms. These form the trigger pulses, which are fed to the HC-SR04 via pin 3 of CON1.

The rest of the circuit monitors the width of the echo pulses sent back from the HC-SR04 via pin 2 of CON1. If this varies significantly (indicating that something has moved between the sensor and the nearest object, like the opposite wall of your entry hall), it sounds the alarm by switching on LED1 and the piezo buzzer connected across it.

This section is a little more complex. First, the incoming echo pulse passes through inverter IC1d, so that its leading edge is negative-going. The 1nF capacitor and 100kΩ resistor then form a differentiator circuit, which develops a narrow negative-going pulse from the negative-going leading edge of the inverted pulse.

This is then used to trigger IC2, a 7555 CMOS timer chip connected as a one-shot multivibrator. When IC2 is triggered, its output pin 3 switches high for a short time, determined by the 2.2μF capacitor connected to pins 6 and 7 to ground and the resistance connected between the same two pins and the +5V line.


As shown, this resistance is the series combination of a 10kΩ resistor

and VR1, a 100kΩ pot. So by varying VR1, we can vary the width of the pulse generated each time the one-shot is triggered.

The output of IC2 is connected to pin 2 of IC3a, one section of a 4070B quad XOR (exclusive-OR) gate. The echo pulses from the HC-SR04 are fed to pin 1 of IC3, the second input of the same XOR gate. Since the output of an XOR gate is high only when one of its inputs is high and the other low, it forms a pulse-width comparator.

Consider the situation where the HC-SR04 sensor is facing a wall, say 1.5m or 150cm away. The echo pulses fed back from the sensor will be very close to 8.7ms wide and these are fed to input pin 1 of IC3a.

 If we adjust VR1 so that IC2 also produces 8.7ms-wide pulses, then since they start at virtually the same instant at the start of the echo pulse, both inputs of XOR gate IC3a will rise and fall at the same time. As a result, the output of IC3a (pin 3) will remain low at all times.



This tiny active piezo transducer module from Jaycar can be used in the intruder alarm instead of the piezo buzzer.

But if someone moves in front of the HC-SR04, this will cause the echo pulses to shorten, because the ultrasonic energy reflected back by the person or object will be travelling over a smaller distance. So the echo pulse width will drop briefly to say 5-6ms, and as a result the inputs of IC3a will no longer be synchronised.

Although the pulses fed to pin 2 will still be high for 8.7ms, the echo pulses being fed to pin 1 will drop low after 5-6ms, so the output of IC3a will switch high for the remaining 2.7-3.7ms. These positive-going pulses will very quickly charge up the 1µF capacitor in the gate circuit of MOSFET Q1, via diode D3 and the 10kΩ series resistor, and this will turn on Q1, causing LED1 to light and the piezo buzzer to sound the alarm.

Then, when the intruding person or object moves away again and the echo pulses return to their original width of 8.7ms, the pulses fed to the two inputs of IC3a will be again be synchronised. There will be no more output pulses from IC3a and the 1µF capacitor will be discharged by the 1MΩ resistor connected across it. So within a couple of seconds, the buzzer and LED will switch off.

The circuit is quite easy to set up, too. All you need to do is wire it up and connect it to the HC-SR04 module using a suitable length of 4-conductor cable. Then mount the sensor module on one side of the hall or doorway you want to monitor, facing either a wall or a large fixed object such as a dresser, a chest of drawers or a filing cabinet.

Next, set pot VR1 to its fully anti-clockwise (ie, minimum resistance) position and turn on the 5V power supply. You'll find that LED1 will immediately light, and if you have a piezo buzzer connected as well, it will sound. That's because the pulses being generated by the one-shot IC2 will be shorter than the echo pulses coming from the HC-SR04.

Now slowly turn pot VR1 clockwise until LED1 turns off and the piezo buzzer goes silent. Your intruder alarm will then be set up and ready to detect the presence of a 'foreign body' in the space between the sensor and its reflecting wall. So we've done all this without a microprocessor – apart from the EM78P153S micro inside the HC-SR04 sensor module itself, of course.

Parts List

1 HC SR04 ultrasonic sensor
 1 active piezo transducer module **OR**
 1 piezo buzzer
 1 100 Ω trimmer pot (R1)

Semiconductors

1 1N4148 diode (D1)
 2 1N4148 diodes (D2)
 1 EBC1235 LED (E1)
 1 220MΩ resistor (R2)
 1 01010 HC1-CM (C1)
 1 1MΩ resistor (R3)
 1 001000µF electrolytic capacitor (C2)
 1 001000µF electrolytic capacitor (C3)

Capacitors (16V)

1 2.2MΩ
 1 1MΩ
 2 100nF
 1 1nF

Resistors (0.25W, 5%)

1 2.2MΩ 1 1MΩ 1 100 Ω
 2 10 Ω 1 1 Ω 1 0 Ω
 1 100 Ω

Reproduced by arrangement
 with SILICON CHIP
 magazine 2018.
www.siliconchip.com.au

FANTASTIC MODERN POWER SUPPLY ONLY IU HIGH PROGRAMMABLE	
AM A E E P E 100 1 100 1 A o ed As e	32
AM A E E P E 0 30 0 30A	32
R 202	900
Maconi 29	800
R AP 2	19
HP332 A	19
HP3 1A	0
HP 032A	0
HP 22A	3 0
HP 2 A	3 0
HP 32	19
HP A	00
HP A	00
HP83 1A	2 000
HP83 31A	1 800
HP8 8 A	12 0
HP8 0A	1 0
HP8 0E	2 2 0
HP8 3A	1 200
HP8	0
HP8 2A	32
Maconi 2022E	800
Maconi 202	0
Maconi 2030	2 0
Maconi 230	29
Maconi 2 0	3 0 0
Maconi 29 /A/	9
Maconi 29	2
Maconi 29 A	1 00
Maconi 200	19 0
Maconi 200A	2 300
Maconi 200	29
Maconi 9 0	29

e t o n i 30 2 / C	scilloscope 00MH 2. /	1 00
e t o n i 3032	scilloscope 300MH 2. /	99
e t o n i 3012	scilloscope 2 Channel 100MH 1.2 /	0
e t o n i 2 30A	scilloscope dual trace 10MH 100M /	3 0
e t o n i 2	scilloscope Channel 00MH	00
a n e l l A P 0 / 0	P 0 0 0 0 A 1 itch Mode	19
a n e l l H 0 / 0	P 0 0 0 0 A	00
a n e l l A 3 / 2	P 0 3 0 2 A ice i t a l	
a n e l l 1	ine/s scillato 10H 1MH	
Racal 1991	Counte / ime 1 0MH 9 i t	1 0
Racal 2101	Counte 20 H E	29
Racal 9300	ue RM Millil oltmete H 20MH etc	
Racal 9300	As 9300	
lu e 9	copemete 2 Channel 0MH 2 M /	
lu e 99	copemete 2 Channel 100MH /	12
i a t o n i c s 100	nthesised i n a l e n e a t o 10MH 20 H	19 0
e a d o a	PA este	9
o l a t o n 1 0 / P	1/2 i t MM ue RM EEE	/
o l a t o n 12 3	ain Phase Anal se 1mH 20 H	00
a s a a o M03 2	P 0 3 0 2 A 2 Mete s	30
h u l P 320 M	P 0 30 0 2 A ice	1 0 200
h u l 210	unction e n e a t o 0.002 2MH etc e n o o d a d e d	
HP33120A	unction e n e a t o 100 mic o H 1 MH	2 0 300
HP 3131A	n i e s a l Counte 3 H o e d u n e d	00
HP 3131A	n i e s a l Counte 22 MH	3 0

R A AR MM
32 R 2 H HA E
A MPER



HP 34401A Digital Multimeter 6 1/2 Digit

E A HP100MH C PE R
R C MP E E HA
ACCE RE 12



HP 54600B Oscilloscope Analogue/Digital Dual Trace 100MHZ

MARCONI 2955B Radio Communications Test Set 800



CA E PP E H P A
RA CA E

PR PER 200MH
A A E C PE 2 0



FLUKE/PHILIPS PM3092 Oscilloscope 2+2 Channel 200MHZ Delay TB, Autosec etc

STEWART OF READING
 1 A in t eet Mo time nea Readin R 3R
 elephone: 0118 933 1111 a : 0118 9331275
 E E EC R C E E PME
 Chec e site www.stewart-of-reading.co.uk
 (ALL PRICES PLUS CARRIAGE & VAT)
 Please check availability before ordering or calling in



HC-SR04 Ultrasonic Sensor Module

HC-SR04 Ultrasonic Sensor is a very affordable proximity/distance sensor that has been used mainly for object avoidance in various robotics projects. It has also been used in turret applications, water level sensing, and even as a parking sensor.





SKU: [SSR-1012](#)

Brief Data:

- Power Supply: 3.3~5 VDC
- Quiescent Current : <2mA
- Working Current: 2.8mA @ 5V
- Effective Angle: <15°
- Ranging Distance : 2cm - 400 cm or 1" - 13ft
- Connector: 4-pins header with 2.54mm pitch.
- Dimension: 45mm x 20mm x 15mm
- Weight 8.5-g.

Using Cheap Asian

Electronic Modules Part 3

  

Computer Interface Modules

Want to connect a microcontroller to your PC? How about interfacing with a microSD memory card? These low-cost modules make life really easy! Jim Rowe shows you how.

THE SECOND MODULE we're looking at this month has been used in a number of recent projects. It's a serial USB-UART (universal asynchronous receiver/transmitter) bridge which allows just about any microcomputer or peripheral module to exchange data with a PC, via a standard USB port.

Let's start by explaining what is meant by the rather clumsy term 'serial USB-UART bridge'. First, a UART is an interface which can operate in one of several different common serial protocols. The serial protocol we're most interested in (and which is most widely used) is 3.3V 'TTL' RS-232. The term 'bridge' simply refers to the fact that this module allows data to pass between the USB interface and UART interface unchanged.

In fact, we've already described a device with essentially the same purpose, the Microchip MCP2200 'protocol converter' used in the *USB/RS-232C Serial Interface* which was published in the April 2015 issue.

Note that for a UART to provide a fully compatible RS-232 serial port, as used in many now-obsolete PCs, it's necessary to provide level shifting from the UART's 3.3V (TTL) signalling levels to the RS-232 bipolar logic levels of $\pm 3-15V$.

But these days, RS-232 is commonly used for short-range communications between microcontrollers and bridges and in this case, the TTL signal levels are all you really need.

The first serial USB-UART bridge modules to become popular were based

around British firm FTDI's improved FT232R converter chips. However, these chips became so popular that some Asian firms made 'clones' of them, even going so far as copying the package markings.

Understandably, this upset FTDI and as a result they released a new version of their Windows VCP driver which was able to identify when a clone chip was being used and disable it. This 'clone killer' driver was included in an automatic update that Microsoft unwittingly provided to Windows users.

As a result, thousands of people found that their low-cost USB-UART converter modules, some inside commercial products, suddenly stopped working and became worthless. Naturally, this made many people cautious of buying any converter based on the FTDI FT232R chip, because of the difficulty in ensuring that you are buying a genuine FTDI chip rather than a clone chip that would stop working as soon as you tried to use it with Windows.

As a result of this, CP2102-based USB-UART bridges have become very popular. These are not only less expensive than FT232-based modules but are (currently) free from such driver issues.


A good example of this type of module is the tiny one shown in the photo to the right. This same module has been used in recent projects and can be used with virtually any Micromite to program the micro as well as debug the software or load data into or out of the micro's RAM.

The CP2102-based bridge

As you can see from the photo and circuit diagram in Fig.1, there's very little in this module apart from the CP2102 chip (IC1), three indicator LEDs and half a dozen passive components.

The internals of IC1's tiny (5 × 5mm) 28-pin QFN SMD package are shown in the internal block diagram, Fig.2. It's conceptually quite simple but involves tens of thousands of logic gates and memory cells as well as carefully designed analogue circuitry.

 The main functional blocks are the USB transceiver at lower left, the USB function controller at lower centre and the UART block at lower right with its full range of data and handshaking inputs and outputs. Notice that there's also an internal 1024-byte EEPROM



A CP2102 module, measuring only 20 × 16mm. Two of the indicator LEDs glow when data is being transmitted.

 


Fig. 1: complete circuit diagram for the CP2102-based serial USB-UART bridge. The CP2102 can be powered directly from the USB V_{BUS} line and it contains a low drop-out voltage regulator to provide 3.3-3.45V (V_{DD}) from 4-5.25V (REGIN).

used to store the USB ID information: the vendor ID, the product ID, the serial number, the power descriptor, the release number and product description strings.

In addition, there are two RAM buffers, one 640-byte USB transmit buffer and one 576-byte USB receive buffer.

Since the CP2102 has a calibrated 48MHz oscillator, it needs no external crystal to operate at the USB 2.0 full-speed rate of 12Mbps. Finally, it contains its own low drop-out (LDO) voltage regulator, to give an output of 3.3-3.45V from an input (REGIN) within the range 4.0-5.25V. This means that it can be powered directly from the USB V_{BUS} line.

Circuit details

While this regulator can supply up to 100mA, the circuitry within the chip itself draws only a little over 26mA (maximum) even in normal operation, and only 100 μ A when suspended. This means it can supply up to 70mA or so for external circuitry needing a 3.3V supply.

In short, the CP2102 is a very impressive chip. Now turn your attention back to the module's circuit of Fig. 1. There's a micro-USB socket at the left (CON1) to connect to a PC's USB port via a standard cable and also to power the module itself. So the V_{BUS} line from pin 1 of the socket connects to pins 7, 8 and 9 of the CP2102, with 10 μ F and 100nF bypass capacitors.

Note that the module does not provide connections to any of the CP2102 UART's handshaking lines, except for DTR ('data terminal ready'). However, this is unlikely to pose a problem for most applications nowadays, since even the DTR line is rarely used.

On the right-hand side there's a 6-way pin header (CON2) for the UART input, output and handshaking (DTR) connections, plus the ground,

+5V and +3.3V power connections for use by external circuitry. There's also a 100nF bypass capacitor on the +3.3V line, plus three small indicator LEDs, each with its own series resistor for current limiting.

LED1 is driven from pin 11 of the CP2102, the SUSPEND output, so it only glows when the device is not suspended by the host PC, ie, when it's communicating with the PC normally via USB. On the other hand, LED2 and LED3 are connected between the +3.3V supply (pin 6) and pins 26 (TXD) and 25 (RXD) respectively, to indicate when data is being sent and received via the bridge.

LED1 draws a little over 1mA when it's operating, while LED2 and LED3 will each draw about 5mA. Thus the LEDs could draw up to 11mA from the 3.3V supply (with full duplex serial communications, allowing LED2 and LED3 to light simultaneously) and this should be taken into account when figuring out how much reserve current is available for external circuitry.

How to use it

Using the CP2102 based USB-UART bridge module is very straightforward. But before you can do so, you

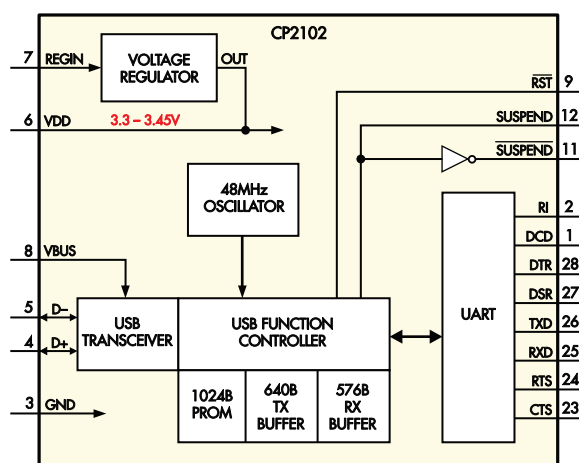


Fig. 2: block diagram for the CP2102. This UART interface implements all RS-232 signals, including those for control and handshaking, although an external level shifter is required for full RS-232 compatibility.

Reproduced by arrangement with SILICON CHIP magazine 2018. www.siliconchip.com.au

may need to install a virtual COM port (VCP) driver on your PC. This is the software which takes care of buffering data to and from the bridge and setting up the UART. In Windows, it makes the UART appear as if it were a legacy COM port.

You can get the right VCP driver from the Silicon Labs website: www.silabs.com/products/interface/Pages/interface-software.aspx

You can also download the latest version of the CP2102 data sheet from: www.silabs.com/support/Pages/document-library.aspx

When you go there you'll find they can provide VCP drivers for not only Windows 7-10, but also for Windows 2000/XP/Vista/Server 2003, WinCE, Mac OS 9 and X, Linux (3.x.x and 2.6.x) and Android. They can also provide drivers for direct 'USB-Xpress' interfacing to the PC, as an alternative to using the VCP approach.

Note that most modern operating systems, including Windows 10 and the latest versions of Mac OS X and Linux, should already have a suitable VCP driver installed. In this case, all you need to do is plug the bridge into a USB port and check that it has been recognised (eg, in Windows, check that a new COM port appears).

Once the driver is installed and working, you can set up your applications to communicate with the module via the new COM port. That includes setting the correct baud rate and other options.

Of course, your circuitry on the UART side of the module needs to be connected to the appropriate pins on header CON2. These will usually be just the RXI, TXO and GND pins, although you might also want to make use of one of the power supply pins as well.

If you aren't sure whether the bridge is working properly, the simplest way to test it is to wire up the RXI pin to the TXO pin. You can then open a terminal emulator, connect to that port

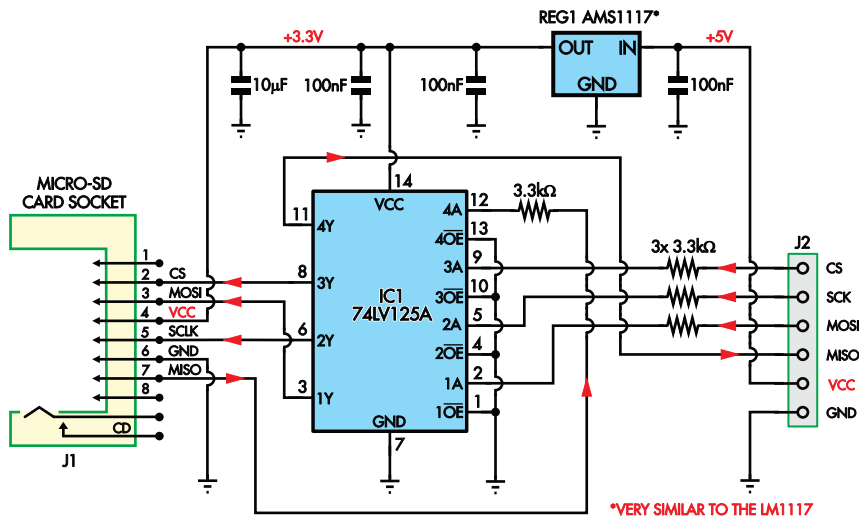


Fig.3: full circuit of the SPI/microSD adaptor module. REG1 reduces the 5V (V_{CC}) input supply from the host module to 3.3V, as required by microSD cards, while IC1 similarly reduces signal levels from the micro (which may run off 5V) to the 3.3V signal levels used by the SD card's I/Os.

and type on your keyboard. The typed characters should be sent back to you and appear in the terminal. If that works, but you still can't communicate with your target device, check that the connections to its TX/RX pins are not swapped and also that you have set the right baud rate.

microSD card interface

There are many different adaptors for accessing an SD memory card from a

microcontroller or embedded module but they generally function in the same manner. The main differences are in terms of the card socket they provide and the chip(s) they use for interfacing.

The full circuit for this module is shown in Fig.3. Note that all SD cards can communicate via either serial peripheral interface (SPI) or a faster method, which consists of either a 4-bit parallel bus (older cards) or a high-speed differential interface

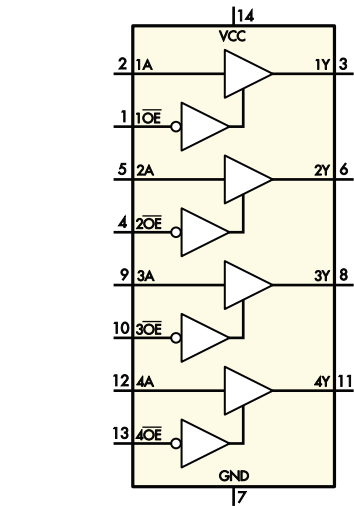



Fig.4: internal block diagram of the SN74LV125A IC. When an OE input is pulled high, the corresponding output is disabled and has a high impedance.

(UHS-compatible cards). The SPI method is by far the simplest to implement with a microcontroller, unless it has a built-in SD card interface.

The other important thing to note is that all SD memory cards are intended to run from a 3.3V power supply and expect logic signals no higher than +3.3V. Some cards can only accept signals swinging over a smaller range, like 0-1.8V (UHS-I) or 0-0.4V (UHS-II).

Glossary

- C Port** PC communications port, normally sending and receiving data using the RS-232 serial protocol.
- CS (Card Chip Select)** used in an SPI bus to indicate when the master wants to communicate with a slave (pulled low).
- R (ata ermina Read)** a 'flow control' signal which is used to indicate when the serial port is ready to receive data. Other, related flow-control signals include DSR (Data Set Ready), CTS (Clear To Send) and RTS (Ready To Send).
- PR (ectrica rasea e, Pro ramma e Read n emor)** non-volatile memory that can be erased and rewritten by applying a higher voltage than is used to read data back. EEPROM is normally more robust than Flash.
- L (o drop out re u ator)** a regulator which can maintain regulation with less than 2V between its input and output.
- icromite:** a Microchip PIC32 programmed with the MMBasic interpreter.
- S (master in, s a e out)** the serial data line used to transmit data from the selected slave to the master in an SPI bus.
- S (master out, s a e in)** the serial data line used to transmit data from the master to the selected slave in an SPI bus.
- (uad at o ead)** a standard series of surface-mount integrated circuit packages. As the name suggests, it is attached to a PCB without through-holes via lands (pads) on the bottom and sides of the package (ie, without leads).
- RS 2 2 or 2 2** one of the most common standards for serial communications. Used by the serial ports on older PCs. Uses one wire for self-clocked data in each direction plus optionally, several flow control signals.
- R or R** serial data receive line. Normally connected to TX or TXD on the other device.
- Seria Communication** the process of transferring data one bit at a time over a communication channel or bus.
- SC (Seria C oc)** the shared clock line in an SPI bus, driven by the master, typically up to 20MHz.
- S (Secure i ita)** a non-volatile portable storage device using Flash memory. Successor to MMC (MultiMedia Card).
- SP (Seria Perip eria nter ace)** a standard serial interface bus, commonly used between a microcontroller and peripherals such as SD cards. Unlike RS-232, SPI has a separate clock line – ie, three wires for bidirectional communications.
- L(ansistor ansistor Lo ic)** refers to digital signals with a 5V or (later) 3.3V amplitude, as used in early digital circuits.
- or data transmission line.** Normally connected to RX or RXD on the other device.
- R (ni ersa s nc ronous Recei er ransmitter)** circuit to handle sending and receiving of serial data using one of several different serial protocols or variations thereof.
- S (ni ersa Seria us)** high-speed serial bus with power (initially using four conductors) which replaced RS-232 and parallel ports for interfacing a PC to pluggable peripherals; from 1.5Mbps up to 5Gbps in latest version.
- S (tra i Speed)** transfer speed for the latest SD cards; up to 104MB/s for UHS-I, and 312MB/s for UHS-II.
- VCP (Virtua C Port)** a device driver that emulates an RS-232 serial port over a different protocol such as USB.

 

This microSD module on a 43 × 24mm PCB is available from the SILICON CHIP online shop at: www.siliconchip.com.au/Shop/7/4019

Just because a chip has an SPI interface doesn't mean it can necessarily interface directly with an SD card. If the micro operates from a 5V supply, its SPI port(s) may well provide and expect logic high signals above +3.3V. This means that the adaptor is needed both to drop the supply voltage down to 3.3V (assuming a suitable rail is not already available elsewhere) and also to act as a logic-level translator for the SPI signals.

The module shown here incorporates LDO regulator REG1 to drop the +5V supply voltage from the micro (via J2) down to the +3.3V needed by both the microSD card at J1, and the single chip (IC1) on the module itself.

IC1 is an SN74LV125A tri-state buffer, to interface between the 5V logic levels (TTL) used on the micro side (via J2) and the low-voltage (0-3.3V) logic levels used on the SD card side (via J1). IC1 operates as a quad non-inverting buffer with tri-state outputs, ie, each output has its own \overline{OE} (output enable low) input; see the internal block diagram of Fig.4. The \overline{OE} inputs are not used, they are all tied to ground to enable the buffers permanently.

If you trace the signal paths through the circuit, you'll see that the three outgoing signal lines from the micro's SPI port at J2 (CS [card select], SCK [serial clock] and MOSI [data; master out, slave in]) each pass through a 3.3k Ω isolating resistor (to reduce ringing and provide some static electricity protection) and then through one of the buffers in IC1 to reach the corresponding pin on SD card socket J1.

For example, the 5V MOSI signal enters via J2, passes through its 3.3k Ω resistor and then goes to buffer input 1A (pin 2). The low-voltage logic version of this signal then emerges from the 1Y output (pin 3) and runs to the MOSI pin of J1, the microSD card socket.

The SCK and CS signals are processed via IC1 buffers 2 and 3 in the same way. The path followed by the MISO (data; master in, slave out) signal is similar, the only difference

being that in this case the signal is travelling from the microSD card at J1 back to the micro at J2. Note though that the circuit does not level-shift this signal to 5V, so the micro will have to cope with a data input signal that only swings up to around 3.3V; most 5V micros are capable of this.

So the hardware side of the module is quite simple. Having said that, the SD card control protocol is quite complicated and so the software required to drive it is far from trivial.

Putting it to use

Since the module simply provides a transparent bridge linking the microSD card to the SPI port of your microcomputer, the software or firmware in the micro can exchange data with the card using the standard SPI commands. So with an Arduino, you can use commands like:

```
SPI.beginTransaction(SPISettings());
receivedVal = SPI.transfer(val);
SPI.end();
```

There's also an Arduino code library built into recent versions of the Arduino IDE, designed especially for reading from and writing to SD cards. It offers commands like begin(), mkdir(), open(), remove(), rmdir(), available(), close(), write() and read().

With a Micromite it's also fairly straightforward, using commands such as:

```
SPI OPEN speed, mode, bits
received_data = SPI(data_to_send)
SPI CLOSE
```

However, the Micromite Plus has built-in library commands specifically intended for reading and writing to SD cards; see the recent articles on Micromite programming.

Useful links

- Information on using standard SPI commands with an Arduino, including some short examples, can be found at: www.arduino.cc/en/Reference/SD
- Details on using SPI communications with a Micromite begin on page 92 of the Micromite manual: <http://geoffg.net/Downloads/Micromite/Micromite%20Manual.pdf>
- An article on the SPI bus is available at: http://en.wikipedia.org/wiki/Serial_Peripheral_Interface_Bus
- Wikipedia also has a very informative article on the many kinds of SD cards, at: http://en.wikipedia.org/wiki/Secure_Digital

PoLabs

For more information or software download please visit 


www.poscope.com/epe

PoKeys Connect, Control



- USB
- Ethernet
- Web server
- Modbus
- CNC (Mach3/4)
- IO
- PWM
- Encoders
- LCD
- Analog inputs
- Compact PLC

Stepper motor drivers Drive

 

- up to 256 microsteps
- 50 V / 6 A
- USB configuration
- Isolated
- up to 32 microsteps
- 30 V / 2.5 A

PoScope Mega1+ PoScope Mega50 Measure



- up to 50MS/s
- resolution up to 12bit
- Lowest power consumption
- Smallest and lightest
- 7 in 1: Oscilloscope, FFT, X/Y, Recorder, Logic Analyzer, Protocol decoder, Signal generator



MicroSD Card Adapter Board

Not just a simple breakout board, this microSD adapter goes the extra mile – designed for ease of use.



SKU: [MDU-1026](#)


Brief Data:

- Onboard 5V > 3V regulator provides 150mA for power-hungry cards.
- 3V level shifting means you can use this with ease on either 3V or 5V systems.
- Uses a proper level shifting chip, not resistors: less problems, and faster read/write access.
- Use 3 or 4 digital pins to read and write 2Gb+ of storage!
- Four #2mm mounting holes.
- Push-push socket with card slightly over the edge of the PCB so its easy to insert and remove.
- Comes with 0.1" right angle header pins so you can get it on a breadboard or use wires.



FT232R USB to Serial/TTL Interface Module

 FT232R is a USB to serial UART interface. A low-cost way to add USB capability to Arduino or other microcontrollers. Use this to give your own breadboard Arduino USB capability for bootloading or downloading sketches. This board includes a DTR pin needed to auto-reset Arduino when downloading to your device.



SKU: [MDU-1066](#)

Brief Data:

- On Board Chip: FT232RL
- Draw out all signal port of FT232RL chip
- RXD / TXD transceiver communication indicator
- USB power supply, can choose 5V or 3.3V, set by jumper
- With over current protection, using 500mA self-restore fuse
- Pin definition: DTR, RXD, TX, VCC, CTS, GND
- Pitch: 2.54mm
- Size: 36 x 18mm (L x W)
- Interface: Mini USB

Measuring Temperature and Relative Humidity

Using Cheap Asian Electronic Modules – Part 4



The AM2302/DHT22 digital temperature and relative humidity (RH) sensing module provides about the simplest way to make a microcontroller project with temperature and RH-sensing capabilities.

by JIM ROWE

Low-cost modules capable of sensing and measuring both temperature and relative humidity (RH) have been available for a few years now.

Initially, these modules appeared as peripherals for Arduino and similar microcomputers, but they soon became an almost standard add-on for just about any micro-based project.

How humidity is measured

Relative humidity is the ratio of the amount of water vapour per volume of air at a particular temperature to the maximum amount of water which can be contained by that volume of air at that same temperature without condensation.

Another way to state this is that RH is approximately the ratio of the actual vapour pressure to the saturation vapour pressure. The saturation vapour pressure depends on the dew point temperature, which is the highest temperature for a given humidity level at which water vapour will condense and form dew.

This means that RH depends on three factors: the amount of water vapour in the air, air temperature and atmospheric pressure at the time of measurement.

Since the module described here measures both RH and temperature, if you assume a fixed barometric pressure (eg, at sea level it is typically close to 1 bar), you can compute the absolute humidity based on these two readings.

Just about all of these temperature/RH sensing modules are based on integrated digital sensors made by Chinese firm Aosong Electronics (based in Guangzhou), which also goes by the name MaxDetect Technology.

What's inside

Most modules currently available use their improved AM2302 sensor, which has alternative names: DHT22 or RHT03.

Aosong/MaxDetect say little about what's inside the AM2302/DHT22/RHT03, but mention that it contains a dedicated 8-bit microcontroller (see Fig.5), a temperature sensor and one RH sensor, the latter being based on a special polymer capacitor.

Curious to know more, I carefully cut away the slotted upper section of the plastic device body. All this achieved was to reveal the two sensors, fitted on the top of a very small PCB (18 × 14mm) which is potted

inside the remaining part of the plastic body (see photo and Fig.6).

The polymer capacitor humidity sensor (Fig.1) works by measuring the relative change in the dielectric constant of the capacitor with varying humidity.

Since the change in value differs between capacitors, sensor calibration is required to provide accurate results.

A thermistor provides temperature sensing. The thermistor used is an NTC (negative temperature coefficient) type, made of a conductive material which decreases in resistance proportionally as the temperature rises.

The microcontroller measures the RH sensor capacitance and the thermistor resistance, and then converts the analogue readings to digital values.

This micro and a number of associated components are mounted on the underside of the PCB; we can't determine their exact configuration as it's impossible to remove the potting without destroying most of the circuit.

However, there is a YouTube video where someone has removed all the components from the device. Some of the pictures from that video are shown in this article, and the link to the video is at the end of the text.

Aosong/MaxDetect state that every AM2302 sensor is temperature compensated and calibrated in an accurate calibration chamber, during or after which the calibration coefficients are saved in the micro's one-time programmable memory.

Considering its low price, the claimed performance of the AM2302 is quite impressive. The RH measuring range is from 0 to 100%, with a resolution of 0.1% and an accuracy of $\pm 2\%$, while the temperature measuring range is from -40 to $+80^\circ\text{C}$ with a resolution of 0.1°C and an accuracy of $\pm 0.5^\circ\text{C}$. The long-term RH stability is rated as $\pm 0.5\%$ per year.

Fig.1: close-up of the humidity sensor, showing the two capacitor plates. Note the darker plate marked with red is much smaller than the gold one underneath.*




 


Fig.2 (below): complete connection diagram for the AM2302/DHT22 sensor module. The $4.7\text{k}\Omega$ pull-up resistor allows for bidirectional communication with a single DATA pin.

 

 

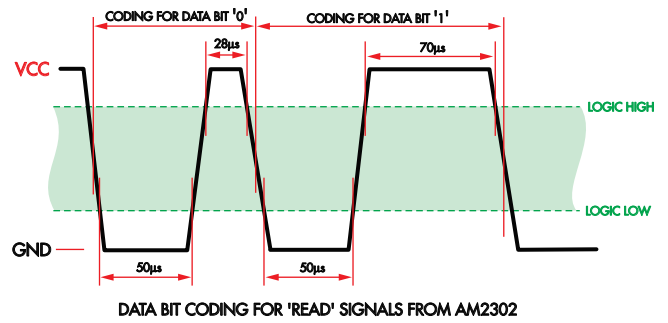FORMAT OF START REQUEST SIGNAL FROM MICRO, 'OK WILL START' RESPONSE FROM AM2302 SENSOR



DATA BIT CODING FOR 'READ' SIGNALS FROM AM2302

Fig.3: to wake the sensor from standby mode, the micro pulls the DATA line low for a minimum of 800µs and a maximum of 20ms. The DATA line then goes high for 20µs. This is regarded as a start request sent to the AM2302.

Fig.4: the micro differentiates between what type of bit it has received based on the pulse time; a data bit of value zero has a pulse time of 78µs while a one has a pulse time of 120µs.

The device is designed to run from 3.3-5.5V DC, with operation from 5V recommended. It has a nominal current drain of 1.5mA when measuring, or 50µA when in standby. It needs at least two seconds between measurements.

The AM2302/DHT22/RHT03 module measures only 25.1 × 15.1 × 7.7mm, while the PCB for the most common module using it measures 39 × 23mm – see our picture.

The sensor has four connection pins, although one is labelled 'NC' (no connection) in Aosong's data sheet.


As you can see from Fig.2, there's very little in a typical sensing module apart from the AM2302/DHT22/RHT03 device itself.

There are just two passive components on the board: a 100nF bypass capacitor from VCC to ground and a 4.7kΩ pull-up resistor between the digital data bus line and VCC.

The reason for that resistor leads us to discuss the way the device communicates with an external micro, over that single-wire bus.

How it handles data

 Although it's poorly explained in the AM2302 data sheet, here's the basic idea: when the DATA line is allowed to float at the logic high level (pulled high by the 4.7kΩ resistor), the sensor effectively sleeps in standby mode. To



The module in question with the case still intact. The module has a fairly low profile, measuring only 7.7mm high.

 


Fig.5 (above): the internal layout of the micro in the AM2302 sensor.*



Fig.6 (right): the sensor module with the top of the case removed. The bead type sensor is an NTC thermistor and to its right is the capacitive humidity sensor.*

wake it up, the external micro must pull the DATA line down to logic low for at least 800µs, but no more than 20ms. In fact, they recommend that it be pulled down for 1ms.

Then the micro should release the DATA line, allowing it to float high again for about 20µs. This '1ms-low-followed-

by-20µs-high' sequence is regarded as the micro sending a start request signal to the AM2302.

If the AM2302 responds to this wake-up call, it pulls the DATA line down to logic low for 80µs, and then allows it to float high again for another 80µs.

This is regarded as its 'OK, will start' response. This 'start request' and 'OK will start' sequence is shown in Fig.3.

Soon after this startup sequence, the AM2302 sends out its current measurement data as a sequence of 40 bits of data, grouped in five bytes – see Fig.7.

 


Fig.7: once there has been a start response from the sensor, the AM2302 sends out its measurement data in 40-bit sets. The first 16 bits is the relative humidity, the 16 bits after is the temperature and the final 8 bits are parity bits to pad the length of the data to 40 bits total.

The relative humidity reading is in the first two bytes (RH HIGH and RH LOW), followed by the temperature reading in the next two bytes (TEMP HIGH and TEMP LOW), and finally there's a checksum or parity byte to allow error checking.

All of these bytes are sent MSB (most-significant bit) first and LSB (least-significant bit) last.

It's also worth noting that both the RH and temperature readings have a resolution of 16 bits.

While this single-wire-bus transaction may look fairly straightforward, it isn't quite that simple – because of the special encoding that Aosong uses for the data bits themselves.

As shown in Fig.4, a binary zero is coded as a logic low of 50µs followed by a logic high of 28µs, whereas a binary one is coded as the same logic low of 50µs, but followed by a logic high of 70µs.

So both a zero and a one begin with a logic low lasting for 50µs, but a logic high that follows lasts for only 28µs in the case of a zero rather than 70µs in the case of a one.

As a consequence, data bits with a value of 0 last for a total of 78µs, while those with a value of 1 last for 120µs. So the time taken by each of those data bytes as shown in Fig.7 will not be fixed, but will vary, depending on the data bit values.

For example, a byte consisting of all zeroes (00000000) will last for only 624µs, while a byte of all ones (11111111) will last for 960µs. So in practice, the duration of each data byte will vary between 624 and 960µs.

The micro connected to the AM2302 needs to take this rather unusual coding system into account when it decodes RH and temperature data.

How it's used

You shouldn't have to worry about decoding the AM2302 measurement data yourself, because many people have already worked it out for most of the popular microcontroller.

For example, if you want to hook up an AM2302-based module to a Micromite, Geoff Graham has already solved this problem and provided a special command in his MMBasic programming language. It looks like this:

HUMID pin, tVar, hVar

Where HUMID is the command keyword and 'pin' is the micro's I/O pin to which the module's DATA line is connected.

'tVar' is the name of the floating-point variable you want to receive the returned temperature (in °C) and 'hVar' is the name of a second

floating-point variable to receive the returned relative humidity (as a percentage). It's that easy!

If you're running the module from a 5V supply, you do have to make sure that you connect the module's DATA line to a Micromite pin that is 5V tolerant – ie, one of pins 14 to 18, 21 or 22 on the 28-pin Micromite.

So if you have connected the module's DATA line to pin 18 of the Micromite and have declared the temperature and RH variables as say 'temp!' and 'RH!' respectively, you'll be able to read the sensor's data with this one-line command:

HUMID 18, temp!, RH!

If you want to take a sequence of say 10 readings spaced apart by the recommended minimum of two seconds and print them to the console, here's the kind of simple program you'll need:

```
DIM nbr% = 10
DIM temp! = 0.0
DIM RH! = 0.0
PAUSE 1000
DO
  HUMID 18, temp!, RH!
  PRINT "Temperature = "temp!
  "C & humidity = " RH! "%"
  nbr% = nbr% - 1
  PAUSE 2000
LOOP UNTIL nbr% = 0
```

If you want to hook up an AM2302-based module to any of the Arduino versions, it's almost as easy. You have quite a choice when it comes to pre-written applications, some of which you'll find using these github.com links:

<http://bit.ly/2DJHJ2O>
<http://bit.ly/2BBraKU>
<http://bit.ly/2BBgju3>

There are also sample programs on both of these websites:

www.aosong.com
www.humidity.com

So it's not at all difficult to use one of these low cost AM2302/DHT22/RHT03-based modules with a readily available microcontroller.

Reproduced by arrangement
 with SILICON CHIP
 magazine 2018.
www.siliconchip.com.au

* These pictures have been
 taken from the video at:

<http://youtu.be/C7uS1OJccKI>

by www.youtube.com/user/electronupdate

PoLabs

For more information or software download please visit



www.poscope.com/epe

PoKeys Connect, Control



- USB
- Ethernet
- Web server
- Modbus
- CNC (Mach3/4)
- IO
- PWM
- Encoders
- LCD
- Analog inputs
- Compact PLC

Stepper motor drivers Drive



- up to 256 microsteps
- 50 V / 6 A
- USB configuration
- Isolated
- up to 32 microsteps
- 30 V / 2.5 A

PoScope Mega1+ PoScope Mega50 Measure




- up to 50MS/s
- resolution up to 12bit
- Lowest power consumption
- Smallest and lightest
- 7 in 1: Oscilloscope, FFT, X/Y, Recorder, Logic Analyzer, Protocol decoder, Signal generator



DHT11 Humidity & Temperature Sensor Module

DHT11 Temperature & Humidity Sensor features a temperature & humidity sensor with calibrated digital output. By using the exclusive digital-signal-acquisition technique and temperature & humidity sensing technology, it ensures high reliability and excellent long-term stability. This sensor includes a resistive-type humidity measurement component and an NTC temperature measurement component with 8-bit microcontroller, offering excellent quality, fast response, anti-interference ability and cost-effectiveness.

 

SKU: [SSR-1006](#)

Brief Data:

- Operating voltage: 3.5~5.5V.
- Humidity Range: 20~90% \pm 5%.
- Humidity Resolution: 1%.
- Temperature Range: 0~50°C \pm 1°C.
- Temperature Resolution: 1°C.
- Operating Current: 3mA (Max).
- Standby: 0.15mA.
- Sampling Period: 1s.
- Mounting Hole: M3.
- 2.54mm breadboard friendly header pin connector.

Using cheap Asian Electronic Modules Part 5

by JIM ROWE

The 'New Blue' 16x2 LCD module with piggy-back I²C serial interface

This module combines a 16x2 backlit alphanumeric LCD module with a small 'piggy-back' module that provides it with an I²C serial interface. This allows it to be hooked up to any of the common micros via only two wires, letting multiple displays (or other I²C devices) share the same 2-wire bus, while also freeing up some of the micro's I/O pins for other purposes.

LCD modules with two lines of 16 characters have been around for many years and we've used them in numerous projects. They are also now much cheaper thanks to their popularity for use with Arduino, Micromite and the Raspberry Pi.

However, many of these Arduino and other microcontrollers are a little limited when it comes to I/O pins, which means that the six or seven pins required to interface to a standard LCD module can leave you with too few pins to interface with other systems and components.

This problem can be solved by using an LCD with a serial interface, or alternatively, attaching a small piggy-back module to a parallel LCD to provide serial/parallel translation.

By using a piggy-back module that communicates using the 2-wire I²C protocol, you end up with an LCD that can be driven using just two wires: one for the serial data (SDA) and the other for the serial clock (SCK). That's apart from the ground and power wires (typically +5V).

What's inside

The circuit of Fig.1 shows the LCD module at upper right, with the rest of the circuitry – the piggy-back, which connects to the module via the usual 16-pin SIL connector – along the top.

All of the serial-to-parallel conversion is performed by IC1, a Philips/NXP PCF8574T device. This is designated as a 'remote 8-bit I/O expander for the I²C bus'. In other words, this IC

accepts serial data over the I²C two-wire bus, via pins 14 and 15, and it makes the data available in parallel format at pins 4-7 and 9-12.

In this case, output pin 4 is used to control the LCD's RS (register select) control pin, while pin 6 controls the EN (enable) pin and pins 9-12 feed the character codes to pins D4-D7 of the LCD. That leaves pin 5 of IC1 to control the LCD's R/W pin, and pin 7 to control the LCD backlight via transistor Q1.

What about pins 1, 2 and 3 of IC1? They're used to set the address of IC1 on the I²C bus. All three pins have 10kΩ pull-up resistors connecting them to logic high (V_{CC}) – but do note that the LCD module PCB also provides three pairs of tiny pads so that any of the pins can be tied to ground.

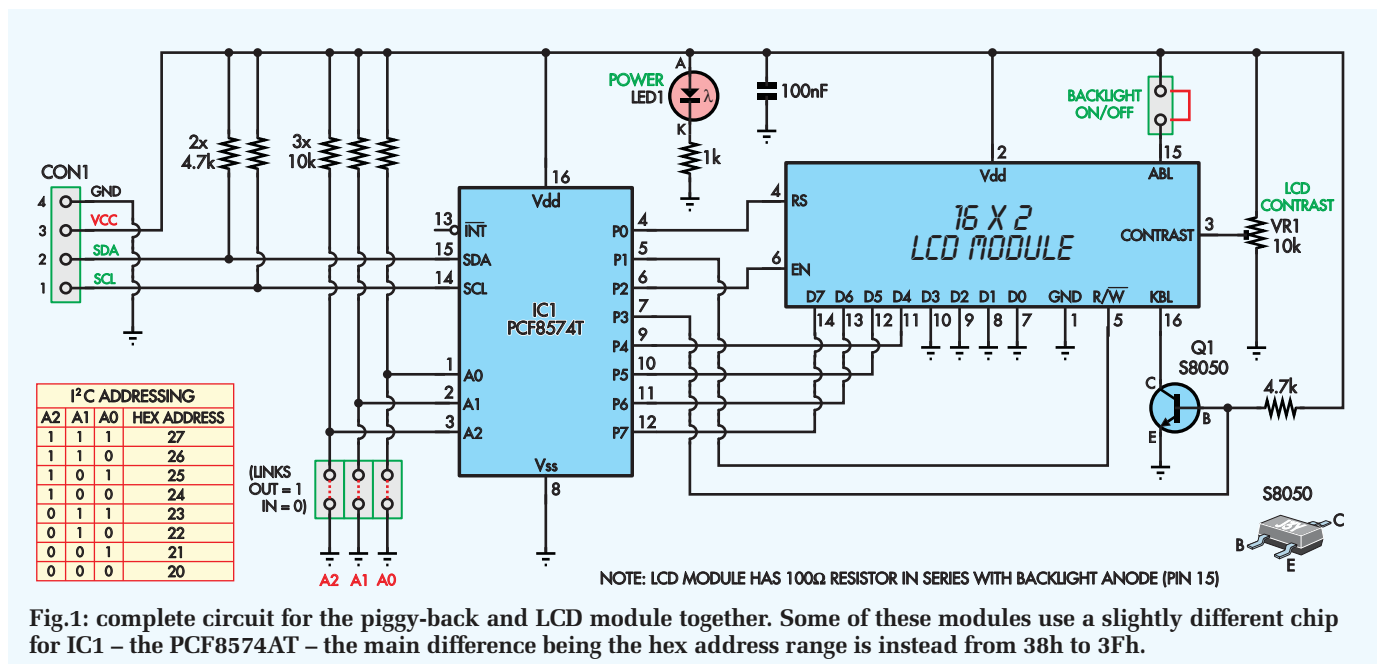


Fig.1: complete circuit for the piggy-back and LCD module together. Some of these modules use a slightly different chip for IC1 – the PCF8574AT – the main difference being the hex address range is instead from 38h to 3Fh.

This allows the chip's I²C address to be set to any hexadecimal value between 0x20 (32) and 0x27 (39), just by bridging the pairs of pads, as shown in the small table at lower left in Fig.1.

So the default I²C address of the piggy-back module (and thus LCD) is 0x27 with all links out, but this can be changed to 0x20 simply by fitting all three links, or to any address in between by fitting one or two links. This allows a number of the LCD-piggyback combinations to be connected to the same I²C bus, with each one given a different I²C address so that the micro driving the bus can send data to any one it chooses.

Other I²C devices can reside on the same bus (eg, temperature sensors, memories, other microcontrollers), as long as you ensure that no two devices have the same address.

There are some serial I²C LCD modules that use a slightly different chip for IC1, the PCF8574AT. This is virtually identical to the PCF8574T shown in Fig.1, except that the I²C address range is between 0x38 and 0x3F.

By using a combination of the two chips, up to 16 different serial I²C LCDs may be connected to the same I²C bus, provided you use eight with the PCF8574T bridge chip and eight with the PCF8574AT chip.

Fig.1 also shows that the piggy-back has a power-on indicator (LED1), a 2-pin SIL connector and jumper shunt that can be used to disable the LCD's backlight if not required. Trimpot VR1 can be used to adjust LCD contrast in the usual way (via pin 3).

Note that the SDA and SCL lines connecting between pins 1 and 2 of CON1 and pins 14 and 15 of IC1 are each fitted with a 4.7kΩ pull-up resistor, as the I²C bus uses active-low logic. These resistors can be left in place if the module is the only slave connected to the I²C bus. However, if you're going to be hooking up other I²C slave devices to the same bus, all but one should have the SDA and SCL pull-up resistors removed.

Using it

This type of module really needs to be hooked up to a micro, and that turns out to be fairly easy to do with any of the popular options available.

All you have to do is connect the V_{CC} and ground pins to a suitable voltage source (which may be the same one that's powering the micro) and the SDA and SCL pins to the I²C bus pins on the microcontroller. Fig.2 shows how this is done with an Arduino Uno or a compatible like the Duinotech Classic. It couldn't be much simpler.

By the way, although the SDA and SCL pins of the LCD module are shown in Fig.2 connected to the

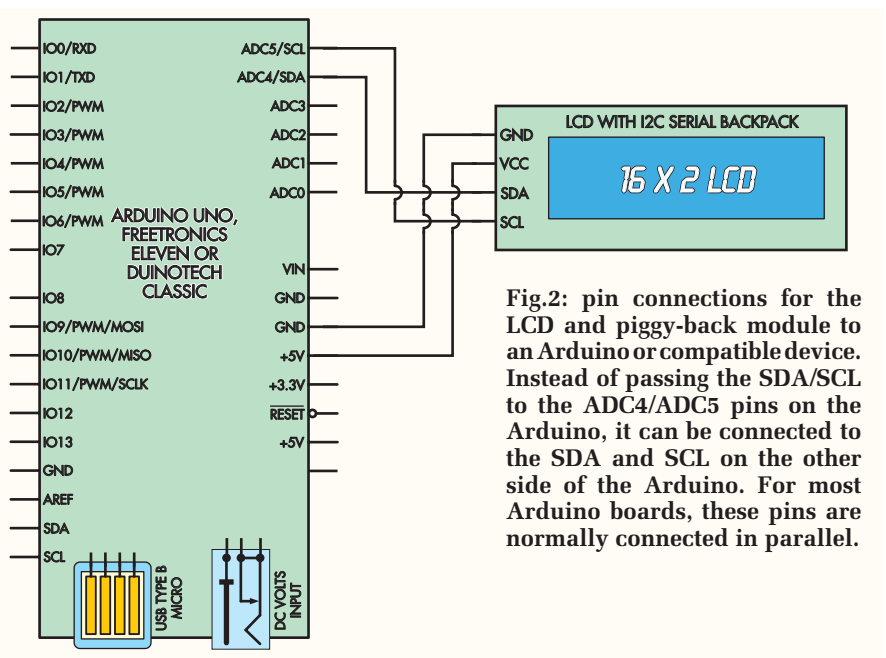


Fig.2: pin connections for the LCD and piggy-back module to an Arduino or compatible device. Instead of passing the SDA/SCL to the ADC4/ADC5 pins on the Arduino, it can be connected to the SDA and SCL on the other side of the Arduino. For most Arduino boards, these pins are normally connected in parallel.

ADC4/SDA and ADC5/SCL pins at upper right on the Arduino, they could instead be connected to the pins marked SDA and SCL on the other side of the Arduino down near the USB connector. On most Arduino boards, these pin pairs are connected in parallel.

It's just as easy to connect the serial I²C LCD module to a Micromite, as you can see from Fig.3.

Connecting the module up to a micro is only half the story. Then you have to work out how to get the micro to send it the data you want displayed.

The complicating factor here is that quite a few people have written 'libraries' to make it easier to drive this kind of serial I²C LCD module from an Arduino sketch, by providing a set of simple function calls like:

```
lcd.print("Text");
```

This is all very well, but even though most of these library files have the name **LiquidCrystal_I2C.h**, they are often different in terms of their finer details and compatibility with any particular serial I²C LCD module.

Rather than you going through the same sort of hassles we did to find a suitable library, we'll simply point

you at some that we found to work. These are available at the following Github links:

<http://bit.ly/2sHf6Cd>
<http://bit.ly/2sLrpxm>

It's possible that these are actually the same library, because in one place we found the author listed as Frank de Brabander but the maintainer as Marco Schwartz. We found both through the following website: www.arduino-libraries.info/libraries/


Anyway, these libraries do seem to work with the module shown, as you'll find out by downloading the 'Hello World' sketch (**HelloWorld.ino**) from the EPE website (www.epemag.com) and running it. We've included a copy of the library (as a ZIP file) within the package. The resulting display is shown in the adjacent photo.

Don't forget to change the I²C address shown in the sketch (0x27) to 0x3F (= 3Fh), if your piggy-back module is fitted with a PCF8574AT instead of a PCF8574T. You'll also have to change this address if you've changed the address using the three small pairs of pads.


Reading hexadecimal numbers

In this article, values prefixed with '0x' correspond to a hexadecimal number; you might also see values suffixed or prefixed with 'h'. Reading from left-to-right, each character corresponds to a 4-bit long value. With 0-9 being equal to themselves and A-F (case-insensitive) equal to 10-15 respectively. A hexadecimal value is calculated as if each character is appended to the other to form one long string of bits.

 Thus, 0x5A (or 5Ah) is equivalent to 01011010 in binary and 90 in decimal form. A string of bits can be read as the sum of each individual non-zero bit, with each bit being equal to 2ⁿ⁻¹ where n is the index of that bit starting from the right. So, 0101 = 0 + 2³⁻¹ + 0 + 2¹⁻¹ = 4 + 1 = 5. A longer example BCDEh would just be equal to 48350 in decimal and 1011110011011110 in binary.



 The top of the LCD module. The screen is mounted on a PCB measuring 80 × 36mm, while the visible area of the LCD measures 64 × 14.5mm.



The underside of the LCD module's PCB has the piggy-back module (black) located above it. The jumper shunt located on the piggy-back module can be used to disable the LCD backlighting if it's not needed.

 


Fig.3: pin connections for the LCD and piggy-back module to a Micromite.

How about a Micromite?

Programming a Micromite to talk to the I²C LCD module is not quite as easy as with an Arduino, as currently the inbuilt MMBasic LCD commands only support the parallel interface. You will find a program called **I2CLCD.bas** in the MMBasic Library, which can be downloaded in zipped-up form from the bottom of this page: <http://geoffg.net/maximite.html#Downloads>

However, this program was written for a piggy-back module with a different configuration than the one which most piggy-backs seem to use (and we have shown in Fig.1). Then there's a further issue in that the I²C command syntax has changed as MMBasic has evolved. As a result, we ended up having to rewrite the software completely.

Changing the program's commands to suit the different connections between the PCF8574T bridge chip and the LCD module itself wasn't too hard. The major difficulty was in getting the program to initialise the LCD's controller correctly.

The correct set-up commands have to be sent to it soon after power is applied, and these commands have to be sent in a particular order, with pauses between them to allow the controller to process them before the next command arrives for correct operation.

After downloading as much information as we could find regarding the correct initialisation sequence and timing for the Hitachi HD44780U and Samsung KS0066U LCD controller chips (which seem to be the two most commonly used in current alphanumeric LCD modules), we were finally able to get the program working correctly and reliably. We found this website most helpful: http://web.alfredstate.edu/weimandn/lcd/lcd/lcd_initialization/

Basically, our program (called **JRI-2CLCD.bas**) just displays a 'Hello, world!' message over and over on the LCD; just like the one for the Arduino. You can download this from our website, open it in MMEdit and then upload it to your Micromite and you should get the same display as shown in the photos.

As with the Arduino sketch, you may need to change the I²C address given for your display's piggy-back, if it has some of the address links fitted or is

using the PCF8574AT chip instead of the PCF8574T. Look for this line near the start:

```
M S N E E 2 dd & 2
' (A2=A1=A0=1)
```

All you need to do is change '&H27' into the correct address for your module. This program provides a good starting point for writing your own MMBasic programs using an I²C LCD. It's fairly well commented, so you should be able to see how to adapt the program to display other things.

Where to buy

We've stocked some of these modules in the Silicon Chip Online Shop so that you can acquire and experiment with them.

Alternatively, you can find similar units (either pre-assembled or as two separate items) on eBay and AliExpress, and also 20×4 character I²C LCDs which cost very little more than the 16×2 types.

The piggy-back should also work with 20×2 and 16×4 size alphanumeric LCDs; however, these are far less popular than the other two sizes.

Serial USB-UART bridge module – another version


Since writing the third article in this series (for the March 2018 issue), we've become aware of another popular version of the serial USB-UART bridge module based on the CP2102 device. This one is very similar to the one we discussed in the March 2018 article, but differs in two respects. One is that instead of a micro-USB socket on the USB end of the module, it is fitted with a full size type A USB plug – providing a more rugged connection and compatibility with a standard USB type A to type A extension cable.

The other difference (wait for it!) is that the connections to the six pins of the SIL connector on the other end of the module are the same as those on the smaller module. So make sure that you allow for the differing SIL pin connections when you connect the module to your micro or other device.

User Guide

I2C to LCD Interface Board

By using this little I2C to LCD interface board, we can control the LCD using only 2 wires, and not worry about resistors to adjust the contrast since it's all included. Usually, Arduino LCD display projects will run out of pin resources easily, especially with Arduino Uno. And it is also very complicated with the wire soldering and connection. This I2C LCD Interface board use an I2C communication interface. It means it only needs 4 pins for the LCD display: VCC, GND, SDA, SCL. It will save at least 4 digital / analog pins on Arduino. All connector are standard 0.1" /2.54mm (Breadboard type). You can connect with jumper wire directly.

 

SKU: [MDU-1042](#)

Brief Data:


- Compatible with Arduino Board or other controller board with I2C bus.
- Interface to HD44780 compatible LCD Modules with various screen size.
- I2C Address:0x20-0x27(0x20 default)
- Supply voltage: 5V
- Interface: I2C to 4bits LCD data and control lines.
- Adjustable contrast
- Board Size: 42x19 mm.



User Guide

I2C Serial Interface 20x4 LCD Module

This is I2C interface 20x4 LCD display module, a new high-quality 4 line 20 character LCD module with on-board contrast control adjustment, backlight and I2C communication interface. For Arduino beginners, no more cumbersome and complex LCD driver circuit connection. The real significance advantages of this I2C Serial LCD module will simplify the circuit connection, save some I/O pins on Arduino board, simplified firmware development with widely available Arduino library.

 

SKU: [DSP-1165](#)

Brief Data:

- Compatible with Arduino Board or other controller board with I2C bus.
- Display Type: Black on yellow green backlight.
- I2C Address: 0x38-0x3F (0x3F default)
- Supply voltage: 5V
- Interface: I2C to 4bits LCD data and control lines.
- Contrast Adjustment : built-in Potentiometer.
- Backlight Control: Firmware or jumper wire.
- Board Size: 98x60 mm.

AD9833-based Direct Digital Synthesiser

Using Cheap Asian Electronic Modules Part 6

R

This little signal generator module uses an Analog Devices AD9833 DDS chip and a 25MHz crystal oscillator. It can be programmed to generate sine, triangle or square waves up to 12.5MHz and it's all controlled via an SPI serial interface.

Direct Digital Synthesiser or DDS chips have been around for well over 20 years now, but for much of that time they were fairly costly.

Until recently, they didn't include an integral DAC (digital-to-analogue converter), so you had to use their digital output to drive a separate DAC to generate the analogue output signal.

In the early 2000s, Analog Devices Incorporated (ADI) announced a new generation of complete DDS devices which did have an integral DAC, as well as offering high performance combined with a price tag significantly lower than what you used to have to pay for a DDS+DAC combination.

Although it's one of the low-cost, lower-performance devices in their range, the AD9833 provides a good example of just what can be achieved nowadays.

When combined with a 25MHz crystal oscillator, it can be programmed to produce any output frequency from 0.1Hz to 12.5MHz in 0.1Hz increments, with a choice of three waveforms: sinusoidal, triangular or square.

All this comes from a chip housed in a tiny MSOP-10 package, running from a supply voltage of 2.3-5.5V, dissipating only 12.65mW and currently with a price tag of around £10 in one-off quantities. That's significantly lower than earlier DDS chips.

As we've seen in previous articles in this series, there has also been a huge surge in the manufacture of many kinds of electronics modules in Asia, especially China, some of them available at surprisingly low prices via internet markets like eBay and AliExpress.

As a result, you can buy the tiny (18 × 13.5mm) AD9833-based DDS module shown in the photos, which

includes a 25MHz crystal oscillator, for the princely sum of £4 each – including free delivery to the UK! That's really quite a bargain, which is why we're focusing our attention on it this month.

To get an idea of how a DDS works, take a look at the panel, *DDS in a Nutshell*, at the end of this article.

Inside the AD9833

The block diagram of Fig.1 shows what's inside that tiny MSOP-10 package. There's quite a lot, although some of the elements are mainly involved in giving the chip its flexibility in terms of output waveform and modulation capabilities. The main sections involved in basic DDS operation are those shown with a pale yellow fill.

Down at lower left in Fig.1 you can see the 16-bit shift register where data and instructions are loaded into the chip from almost any micro, via a standard SPI (Serial Peripheral Interface) bus. We'll discuss that in more detail later.

Just above the serial input register is the control register, also 16-bit. This stores the control words, used to set up the configuration of the device, including the output waveform type, which of the two 28-bit frequency registers (FREQ0 or FREQ1) is used to set the DDS output frequency and also whether the phase is shifted by the content of 12-bit phase registers PHASE0 or PHASE1.

The main reason why the AD9833 has two frequency registers and two

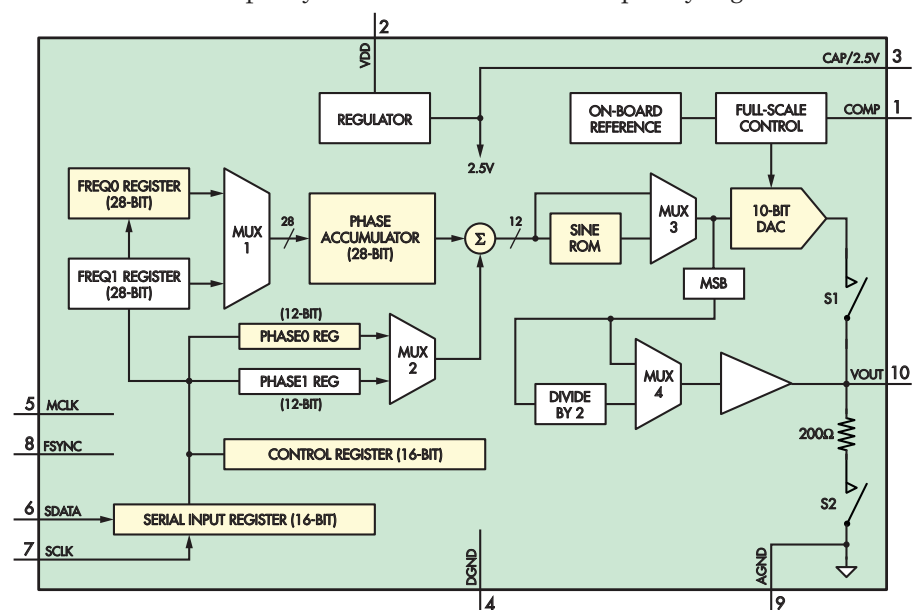


Fig.1: block diagram of the AD9833 DDS IC. The critical blocks are yellow. The phase accumulator generates a series of addresses to look up in the ROM sine table and the resulting values are then fed to a 10-bit DAC which produces the output waveform. Other circuitry allows the output waveform to be changed to a triangle or square wave and also allows for frequency and phase shift keying.

phase registers is to give it the capability of generating signals with frequency-shift keying (FSK) or phase-shift keying (PSK) modulation. Multiplexers MUX1 and MUX2 allow these options to be controlled using bits in the control register.

So how are those 28-bit frequency/phase increment registers $FREQ0$ and $FREQ1$ loaded with 28-bit data from the 16-bit serial input register? This is done by sending the data in two 14-bit halves, in consecutive 16-bit words from the micro, with the lower half first and then the upper half.

The AD9833 can be configured to accept the data this way simply by manipulating two bits in the control register. The same bits can also be used to configure it for setting either the lower or higher 14-bit ‘half word’ alone, which can be useful for some applications (such as frequency sweeping).

MUX3, MUX4 and switches S1 and S2 are all controlled by further bits in the control register. MUX3 simply allows the sine ROM to be bypassed, with the output from the phase accumulator fed directly to the DAC. This is how the AD9833 produces a triangle wave output, since the amplitude of a triangle wave is a linear function of its phase.

For a square wave output, the DAC is disconnected from the chip’s analogue output (pin 10) using integrated switch S1, and instead makes use of the MSB (most-significant bit) output of MUX3. This automatically gives a square wave output and MUX4 allows you to divide its frequency by two, if needed.

The integrated 200Ω resistor connected between the analogue output pin and ground via switch S2 is used to convert the DAC’s output current into a proportional voltage output. Since S2 is controlled in parallel with S1, this means that when S1 cuts the link between the DAC output and pin 10, S2 also removes the built-in 200Ω output shunt.

This makes the chip’s output voltage swing in square-wave mode significantly higher than for the sine or triangular (DAC-derived) options.

To be specific, the square wave output is around 5.2V peak to peak, while for sine or triangular waves the output drops to around 650mV peak-to-peak.

The complete module

Now refer to Fig.2, which shows the complete circuit for the $18 \times 13.5\text{mm}$ module shown in the photo opposite.

It simply comprises the AD9833 DDS chip (IC1) and its equally tiny ($3 \times 2.2\text{mm}$) 25MHz crystal oscillator. There are six even smaller SMD

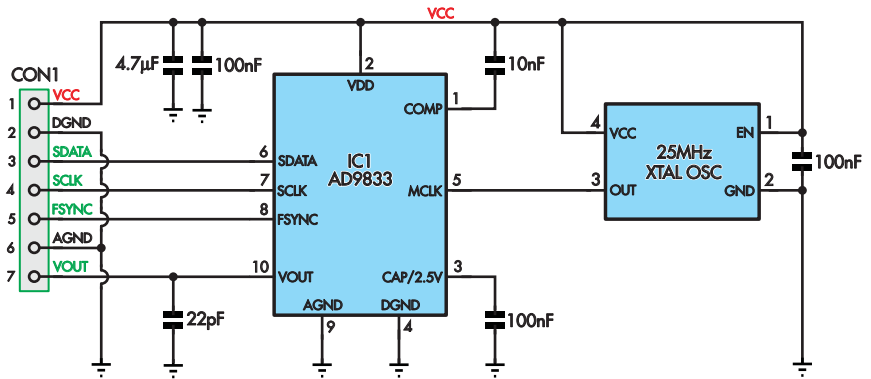


Fig.2: circuit of the AD9833-based DDS module used in this article. The AD9833 IC and 25MHz crystal oscillator plus a few passive components are mounted on a small PCB, with a SIL header to make control and output connections.

capacitors, most of them used for filtering either the power supply rails or IC1’s V_{OUT} pin.

Seven-way SIL connector CON1 is used to make all of the signal and power connections to the module. Pins 1 and 2 are used to provide the module with 5V power, while pins 3-5 are used to convey the SPI commands and data to IC1 from the micro you’re using to control it. And pins 6 and 7 are used to carry the analogue output signal from IC1 out to wherever it’s to be used.

Limitations

Before we talk about driving the module from a micro like an Arduino or a Micromite, we should discuss its limitations.

First, the aforementioned difference in output amplitude for square wave versus sine/triangle waves is a factor of about eight times, or 18dB. So if you want to use the module as the heart of a function generator, you will need to attenuate the square wave output by 18dB, to match the sine and triangle output levels.

You will also need to pass the sine and triangular outputs through a low-pass filter with a corner frequency of around 12-15MHz, to remove most of the DAC switching transients. After this processing, the outputs can all pass through a common buffer amplifier and output attenuator system.

You don’t need to worry about any of these niceties if you simply want to use the module as a programmable clock signal source. You can just program it to generate a square wave output and use it as is.

Another limitation, as noted in the *DDS* in


a *Nutshell* box, is that the maximum output frequency is half the sampling clock frequency; in this case, 12.5MHz. But because of the way a DDS works, it can only produce a clean square wave at this maximum frequency.

If you want to get a reasonably smooth sine or triangular wave output, this will only be possible at frequencies below about 20% of the clock frequency, or in this case, a maximum of about 5MHz.

Programming it


When your program starts up, it will need to carry out a number of set-up tasks. These include:

 1. Declare the micro’s pins to be used by the SPI interface and set them to their idle state (typically high).
2. Start the SPI interface, configured for a clock rate of say 5MHz, the data to be sent MSB (most-significant bit) first and using clock/data timing mode 2 (10 binary). If possible, it should also be set for the data to be exchanged in 16-bit words rather than bytes.
3. Send initialisation commands to the AD9833 to set up its control register, the $FREQ0$ register and the $PHASE0$ register. These involve sending the




The DDS module is shown at approximately twice actual size to provide greater clarity. From left to right, the pin connections are VCC, DGND, SDATA, SCLK, FSYNC, AGND and VOUT.


AD9833 SERIAL INPUT WORD FORMAT:

 



TO WRITE TO THE CONTROL REGISTER:

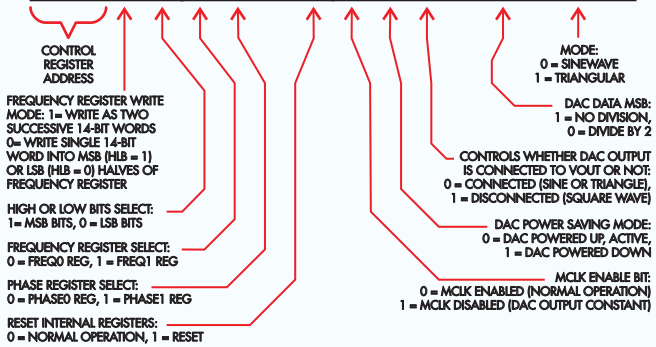

TO WRITE TO A FREQUENCY REGISTER:

 


TO WRITE TO A PHASE REGISTER:

  

Scope 1 (above): a 1000Hz sine wave generated using an Arduino programmed with AD9833_DDS_module_test.ino

Fig.3 (left): the format of the 16-bit digital control data sent to the AD9833. The top two bits determine whether the remaining 14 bits are used to update the frequency, phase or control registers. The control register is used to change the output waveform type, switch between two different sets of frequencies and phases or go into a low-power sleep mode.

 The underside of the DDS module with the 7-pin male header attached. Again, it's shown twice actual size, due to its small size (18 x 13.5mm).



following five 16-bit words (shown here in hexadecimal):

- 0x2100 (resets all registers, sets control register for loading frequency registers via two 14-bit words)
- 0x69F1 (lower word to set FREQ0 for 1000Hz)
- 0x4000 (upper word to set FREQ0 for 1000Hz)
- 0xC000 (writes 000 into PHASE0 register)
- 0x2000 (write to control register to begin normal operation)

With that, the DDS should produce a 1000Hz sine wave. To change to one of the other waveforms, you need to send the correct code to the control register. To change the output frequency, you need to send the appropriate pair of 14-bit words to one of the frequency registers. Note that these are sent lower word first, then upper word.

To make programming the AD9833 a little easier, the basic coding for the control, frequency and phase registers is summarised in Fig.3. I also have written a couple of simple example programs to illustrate programming

the AD9833 module; more about these shortly. First, you'll need to know how the module can be connected to one of the popular micros.

Driving it from an Arduino

Fig.4 shows how to connect the module up to almost any Arduino or Arduino clone.

This takes advantage of the fact that most of the connections needed for interfacing to an SPI peripheral are made available on the 6-pin ICSP header that is fitted to most Arduino variants.


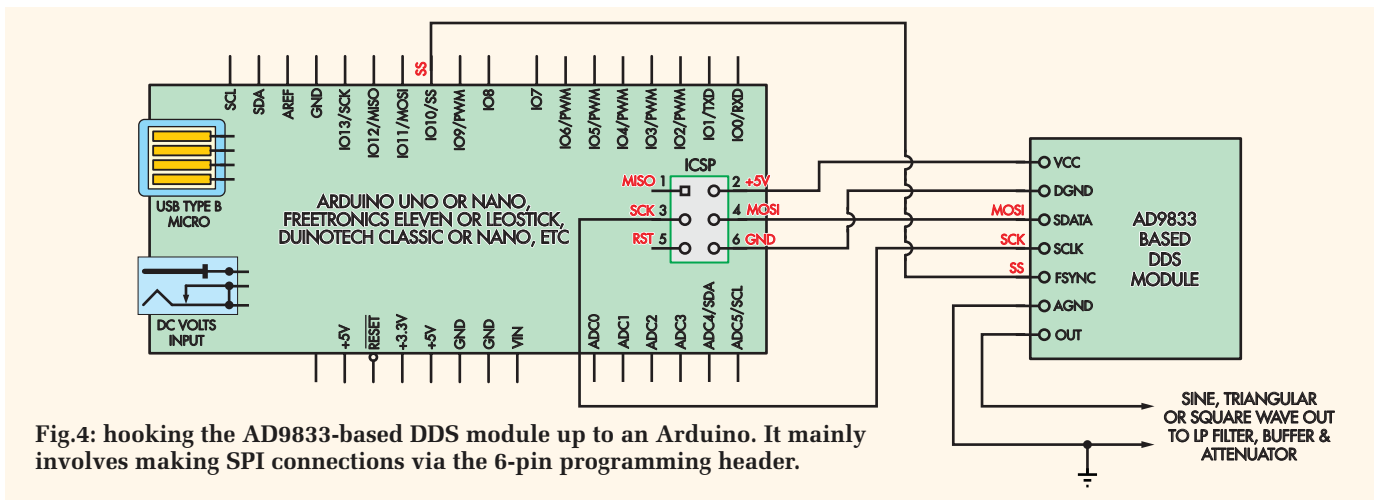
 


Fig.4: hooking the AD9833-based DDS module up to an Arduino. It mainly involves making SPI connections via the 6-pin programming header.

 

Scope 2 and 3: a 1000Hz triangular (left) and square (right) wave produced by running the AD9833_DDS_module_test.ino file on an Arduino or compatible device. Note the higher amplitude of the square wave output.

The connections to the ICSP header are quite consistent over just about all Arduino variants, including the Uno, Leonardo and Nano, the Freetronics Eleven and LeoStick, and the Duinotech Classic or Nano.

In fact, the only connection that's not available via the ICSP header is the one for SS/CS/FSYNC, which needs to be connected to the IO10/SS pin of an Arduino Uno, Freetronics Eleven or Duinotech Classic, as shown in Fig.4.

With other variants, you should be able to find the corresponding pin without too much trouble. Even if you can't, the pin reference can be changed in your software sketch to match the pin you do elect to use.

Arduino sample program

One of my sample programs written for an Arduino is called, **AD9833_DDS_module_test.ino**

It simply initialises the AD9833, starts generating a 1000Hz sinewave (Scope 1) and then changes the waveform after five seconds, giving you a triangular wave (Scope 2), then a square wave (Scope 3) and finally a half-frequency square wave, before returning to a sinewave and repeating the sequence. If you look at the code, you can see just how easy it is to control an AD9833 DDS module from an Arduino.

Driving it from a Micromite

Fig.5, on the next page, shows how to drive the module from a Micromite. By connecting the MOSI, SCK and SS/FSYNC lines to Micromite pins 3, 25 and 22 as shown, MMBasic's built-in SPI protocol commands will have no trouble in communicating with the module.

One thing to note is that if you want to drive the AD9833 module from a Micromite in a *BackPack* that is already connected to an LCD touchscreen, there's a small complication

arising from the fact that the LCD touchscreen also communicates with the Micromite via its SPI port.

To prevent a conflict, your program needs to open the SPI port immediately before it sends commands or data to the module, and then close the port again immediately afterwards.

Micromite sample program

My other program is written for the Micromite, specifically, the Micromite *LCD BackPack*. It's called, **Simple AD9833 FnGen.bas**

This one is a little more complicated and lets you control the AD9833's output frequency as well as the waveform, simply by using buttons and a virtual keypad on the Micromite's touch screen. It's quite easy to drive, and again, should show you how the AD9833 can be controlled via a Micromite.

Both this program and the Arduino program are available for download from the *EPE* website.

Alternative module

In the April issue, we published a Micromite-based *DDS Function Generator* project by Geoff Graham, which also uses the AD9833. Geoff has used a slightly different module which includes the ability to vary the output level and also has a low-impedance buffered output.

The module Geoff has used is shown overleaf, to the left of its circuit diagram, Fig.6. It differs from the simpler module in that it has the output signal from the AD9833 fed to a separate SIL connector.

From there, the signal is routed to an MCP41010 10kΩ digital potentiometer IC via a 0Ω resistor, which acts as a digitally controlled attenuator. The output of this attenuator is fed to an AD8051 rail-to-rail op amp and together these constitute a PGA, or 'programmable gain amplifier' (not pin grid array).

The digital pot also communicates via SPI, and in fact its clock and data pins are wired up in parallel with the AD9833's, so it is on the same SPI bus.

The only difference in communication is rather than pulling the FSY pin low, as you do to communicate with the AD9833, you pull the CS pin low to communicate with the MCP41010.

Like the AD9833, the MCP41010 is controlled by writing 16-bit data words to it. For the MCP41010, the bottom eight bits of the data are the new potentiometer position, while the upper eight bits contain two command bits, two channel selection bits and four 'don't care' bits, which it ignores.

The command bits allow you to select whether you are setting the pot wiper position or commanding the IC to go into a power-down mode.

We suggest you check its datasheet for details; however, you really only need to send one of two different commands to this device when using this module:

0x11xy – set wiper position to 8-bit value xy

0x2100 – shut down potentiometer, saving power and disabling the output signal

For example, the command 0x11FF will set the output level to maximum, command 0x1180 will set the output level to 50% and 0x1101 will set it to the minimum non-zero level.

The attenuated output signal is available at pin 6 and this goes to the non-inverting input of an AD8051 high-frequency op amp, which is configured with a gain of six times, providing an output swing of around 3V peak-to-peak for sine and triangle waves. This signal is fed to both a 2-pin header connector and SMA socket via another 0Ω resistor.

Other variations in this module are that it has 100Ω protection resistors for the four control pin inputs, the

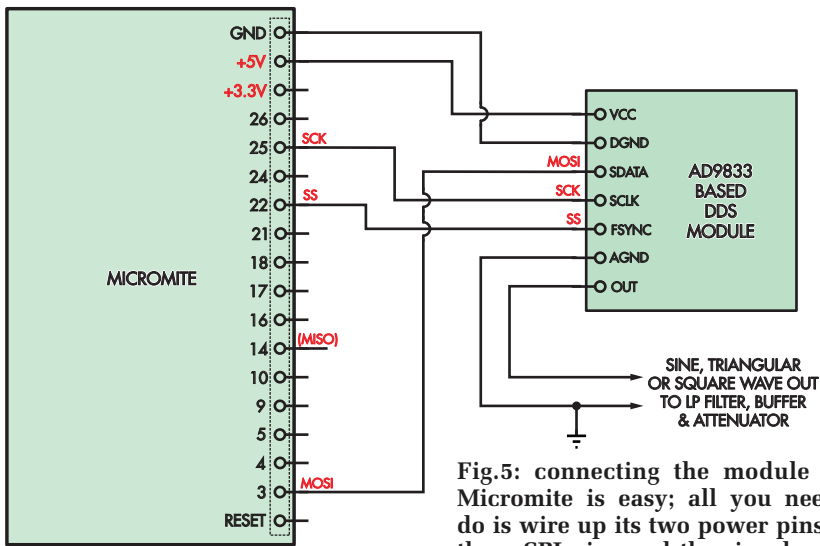


Fig.5: connecting the module to a Micromite is easy; all you need to do is wire up its two power pins, the three SPI pins and the signal output connections.

supply for the 25MHz crystal oscillator has a 10Ω isolating resistor that also forms a low-pass filter in combination with the added 4.7μF ceramic capacitor, and there is a 2-pin header which makes the output of the

AD9833 available, before it enters the attenuator.

There are more details on how to use this module in April's article on the Micromite-based *DDS Function Generator*, but besides needing to program the

digital pot with the attenuation value, its control is pretty much identical to the description above.

Final comments

Dan Amos has designed a 'Touchscreen Function Generator' using an AD9833 module driven by a Micromite with an *LCD Back-Pack*, and he has also added a digital potentiometer, an output buffer amplifier and even an incremental encoder for adjusting either the output frequency or its amplitude.

He has provided the MMBasic source code for his program, and a user manual as a PDF file – both of which can be downloaded from the *EPE* website. That project and its software is an excellent example to get you started on using the AD9833 DDS module.

One last comment – as well as being able to generate fixed frequency, FSK and PSK modulated signals, the AD9833 can also be programmed to generate swept-frequency signals.

In fact, the Micromite *DDS Function*

Direct Digital Synthesis (DDS) in a nutshell

This simplified explanation should give you some insight into how a DDS works. A DDS is based around one or more look-up tables stored in read-only memory (ROM). These contain a set of high-resolution digital samples of a single wave cycle.

Let's consider the case where the table contains a sine wave.

The values from the ROM table are fed to a DAC (digital-to-analogue converter), so that for each entry in the table, the DAC will produce an analogue DC voltage corresponding to the value of the sample stored in that address.

As a result, if a counter is used to cycle through the table entries continuously, the DAC output is a continuous sinewave.

Let's say the table contains 1000 entries which represent a single sine-wave cycle and the counter which indexes the table is incremented at a rate of 1MHz. This means that the output will be a sinewave at $1\text{MHz} \div 1000 = 1\text{kHz}$. By changing the rate at which the counter increases, we can change the output frequency.

Since the DDS chip operates from a fixed external clock, in order to vary the rate at which the DDS runs

through its ROM table, a fancier counter configuration known as a 'phase accumulator' is used. This is shown in Fig.7 and it consists of a binary adder feeding an accumulator register.

The important point to note is that the phase accumulator register has 28 bits of precision while the sample table, with 4096 entries, only requires a 12-bit number to index its entries.

Hence there are an additional 16 bits of fractional phase data in the register and these effectively indicate output phase values in-between those represented by the values in the table.

The binary adder has two 28-bit inputs, one of which is the current phase value from the accumulator register. The other input comes from the frequency register at far left, also 28 bits wide.

This is the register which we use to set the DDS output frequency. At each clock cycle, the value in the frequency register is added to the value in the accumulator register and this result is stored back in the accumulator register. As a result, as long as the frequency register value doesn't change, the accumulator register increases by the same amount on each clock cycle.

With a 28-bit phase accumulator register, a value of zero indicates a

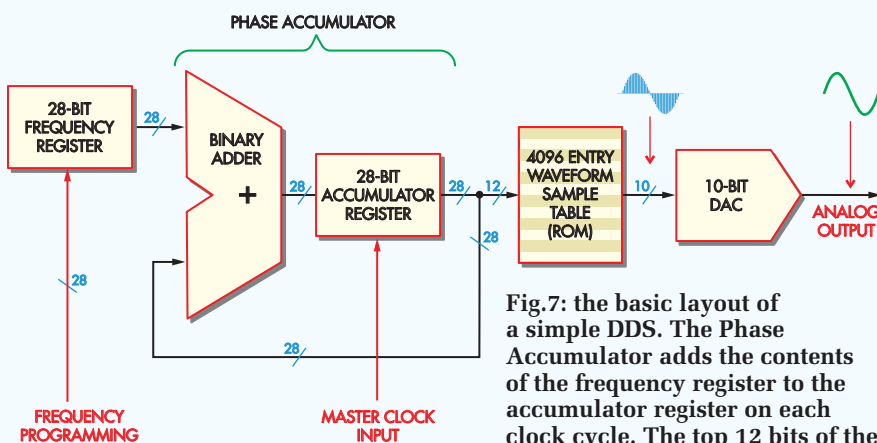


Fig.7: the basic layout of a simple DDS. The Phase Accumulator adds the contents of the frequency register to the accumulator register on each clock cycle. The top 12 bits of the accumulator register is then used

to look up an entry in the waveform table ROM, producing a 10-bit digital amplitude value which is subsequently fed to the digital-to-analog converter (DAC) to generate the analog output signal.

Generator in April's issue does just that, so refer to that article for more details on frequency sweeping.


 


Fig.6: the circuit of the alternative DDS module shown above, which is also widely available. This one incorporates an MCP41010 digital potentiometer to allow the output amplitude to be controlled as well as an AD8051 high-speed op amp buffer to keep the output impedance low and provide some gain to allow a higher maximum output signal level. The module is shown at approximately 1.5 times its actual size of 32 × 32mm.

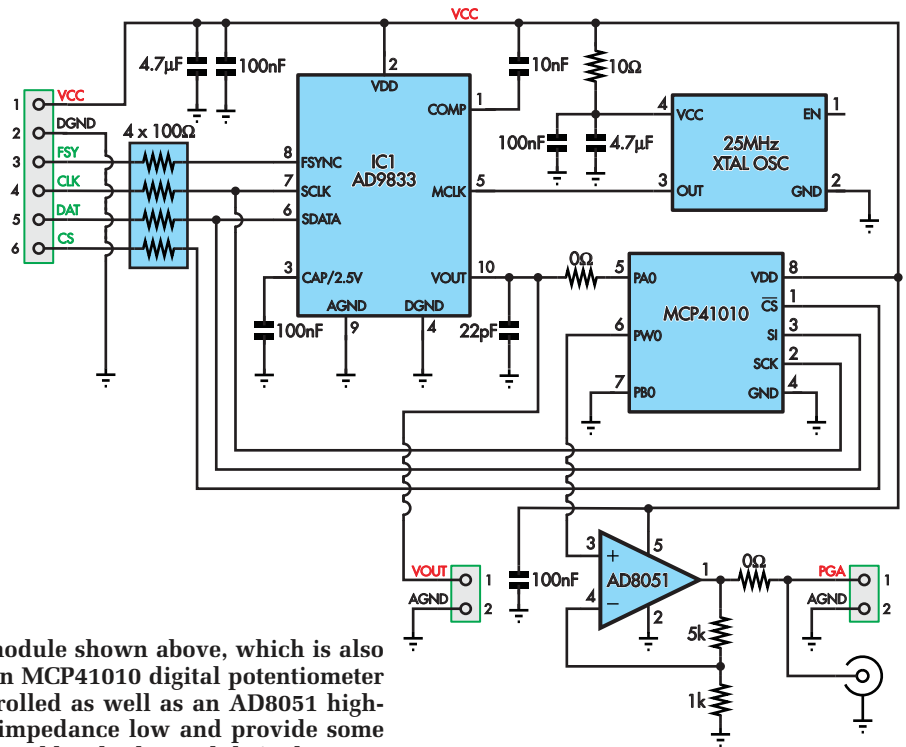

phase in radians of zero while its maximum value of $2^{28} - 1$ (268,435,455) represents a phase of just under 2π .

When the value of the accumulator register exceeds $2^{28} - 1$, it rolls back around to zero, hence maintaining $0 \leq \text{phase} < 2\pi$. Each time it 'rolls over', that represents one complete cycle from the output.

With a frequency register value of 1, it will take 2^{28} clock cycles for this to happen. With a master clock of 25MHz, that means the output frequency will be $25\text{MHz} \div 2^{28} = 0.09313\text{Hz}$ or just under 0.1Hz.

With a frequency register value of 2, it will take $2^{28} \div 2$ clock cycles to roll over, giving an output frequency of $25\text{MHz} \div 2^{27} = 0.186\text{Hz}$ and so on. So the output frequency resolution with this configuration is just under 0.1Hz.

But how are such low frequencies possible with only a 4096-entry table? Well, only the top 12 bits of the 28-bit accumulator register are used to index the ROM table.

This means with the minimum frequency value of one, it will only roll over to the next entry in the table once every $2^{(28-12)} = 65,536$ clock cycles. Hence, each value from the table is sent to the DAC 65,536 times before progressing to the next one, giving a very low frequency.

At higher frequencies, in this case above $25\text{MHz} \div 4096$ (6.103kHz),

values in the table will be skipped when necessary in order to increase the output frequency. In other words, the counter which indexes the table may increase at a rate of 1, 2, 3, 4 times per clock, or somewhere in-between, by skipping the occasional table entry.

For example, to produce an output of 12.207kHz, every second entry from the ROM table is sent to the DAC ($12.207\text{kHz} = 25\text{MHz} \div [4096 \div 2]$).

Based on the above, we can calculate the output frequency as:

$$h \quad \text{cl} \quad \text{Rac}$$

For the DDS shown in the diagram, with a 28-bit phase accumulator having a resolution (R_{ac}) of 2^{28} ($= 268,435,456$) and with a master clock frequency (M_{clk}) of 25MHz, this simplifies down to:

$$h$$

(We're showing the table with 4096 entries, but note that due to symmetry, it is only necessary to store the values representing a quarter of a sine wave.)

The second quadrant of a sine wave is a mirror-image of the first, so this can be achieved by running through a quarter sine table backwards, while the third and fourth quadrant are simply an inverted version of the first and second, and these can be obtained by negating the

values from the first two quadrants.

You'll also notice that the samples stored in the ROM are shown as having a resolution of 10 bits, to suit the 10-bit DAC, which can produce an analogue output with 1024 different voltage levels.

One more thing to bear in mind. Because a DDS achieves higher output frequencies by skipping samples in the waveform ROM, at higher output frequencies, the sampling resolution effectively drops.


This continues until you reach the 'Nyquist frequency' of half the master clock frequency (ie, 12.5MHz) above which the output from the DAC actually starts to drop in frequency.

So the theoretical maximum frequency for a DDS is half that of the master clock.

But in practice, because of the above, if you want a reasonably smooth sine wave output that doesn't need too much low-pass filtering, it's a good idea to limit the maximum output frequency to about 20% of the master clock frequency; say 5MHz for a 25MHz master clock.

Reproduced by arrangement
with SILICON CHIP
magazine 2018.
www.siliconchip.com.au

SPI 8x8 LED Matrix Display Module

 


Using Cheap Asian Electronic Modules Part 7: by Jim Rowe

This low-cost module uses a Maxim MAX7219 serial LED display chip and comes complete with a plug-in 8x8 LED matrix display. However, the MAX7219 is equally capable of driving an 8-digit 7-segment LED display, and its SPI interface allows it to be driven by a microcontroller using only three wires, meaning both the module and the chip are surprisingly flexible.

When I first noticed this type of 8x8 LED matrix display module being offered on eBay and AliExpress, I must confess that I didn't get overly excited. Sure, they were very cheap – but what could you actually use an 8x8 LED matrix display for? All I could think of was displaying a few pretty patterns. Fun, perhaps, but not all that useful.

Despite this ho-hum first impression, I decided to order a couple of the modules just to see if they had any other uses. And when they arrived, I discovered that they did.

 The data sheet for the MAX7219 controller chip is available from Maxim's website (<http://bit.ly/2I5Rz1Q>) and indicates that it has primarily been designed to drive an 8-digit 7-segment LED display. In fact, the ability to drive an 8x8 LED matrix is in many ways just a bonus feature!



This very cheap module includes the MAX7219 IC and a plug-in 8x8 LED matrix display.

Inside the MAX7219

To understand the dual personality of the MAX7219, take a quick look at the block diagram in Fig.1. As you can see, there's more inside this modest-looking 24-pin DIP device than you might have expected.

Down at the bottom, you can see the 16-bit shift register where data and instructions are shifted into the chip from almost any micro, via a standard SPI (Serial Peripheral Interface) bus. Above the eight least-significant bits (D0-D7) is an eight-byte dual-port SRAM, where the display data is stored.

Four more bits, D8-D11, are decoded to determine whether the data in the lower eight bits of the shift register is to be loaded into one of the addresses in the display SRAM (either with or without further decoding), or into one of the control registers to set the chip's operating modes.

Five registers control shutdown, the mode, intensity, scan limit and display test.

The shutdown register blanks the display when power is first applied or at a later time, to reduce the power consumption. It can also be used to flash the display on and off, for 'alarm' situations. During normal operation, data bit D0 of this register is set to one.

The mode register is used to control whether the data in the SRAM registers for each digit is to be decoded (according to 'CODE B') or used as-is. The interesting point here is that the

mode register can be set for decoding all eight digits, none of them or virtually any combination in between.

So for driving an 8x8 LED matrix, for example, you wouldn't use the decoding features, while for driving an 8-digit 7-segment display you'd program it to decode all eight registers.

But you could also use it to drive a 6-digit 7-segment display by decoding just those six digits, with the remaining two digit positions either unused or used without decoding to drive other indicator LEDs. So it's quite flexible.


The intensity register provides programmable digital control over the brightness of the LEDs. As you can see from Fig.1, the chip has a segment current reference circuit (at upper left), controlled by the current fed in via the I_{SET} pin (pin 18).

The peak current sourced from the chip's segment driver outputs (upper right) is nominally 100 times the current entering the I_{SET} pin, which is normally connected to the +5V supply rail via a resistor of 9.53kΩ or more. The module shown in the pictures uses a 10kΩ resistor.

At the same time, the value stored in bits D0-D3 of the intensity control register determines the duty cycle of the chip's internal pulse-width modulator, and hence the display brightness. The duty cycle is a 4-bit value, meaning that there are 16 different programmable duty cycle/brightness levels, from 1/32 (3%) to 31/32 (97%).

A WHEN DATA BIT 'CODE B DECODE' MODE IS SELECTED

DATA BITS										
DP	D7	D6	D5	D4	D3	D2	D1	D0		
(DP)	X	X	X	X	0	0	0	0	(X0 hex)	0
(DP)	X	X	X	X	0	0	0	1	(X1 hex)	1
(DP)	X	X	X	X	0	0	1	0	(X2 hex)	2
(DP)	X	X	X	X	0	0	1	1	(X3 hex)	3
(DP)	X	X	X	X	0	1	0	0	(X4 hex)	4
(DP)	X	X	X	X	0	1	0	1	(X5 hex)	5
(DP)	X	X	X	X	0	1	1	0	(X6 hex)	6
(DP)	X	X	X	X	0	1	1	1	(X7 hex)	7
(DP)	X	X	X	X	1	0	0	0	(X8 hex)	8
(DP)	X	X	X	X	1	0	0	1	(X9 hex)	9
(DP)	X	X	X	X	1	0	1	0	(XA hex)	-
(DP)	X	X	X	X	1	0	1	1	(XB hex)	E
(DP)	X	X	X	X	1	1	0	0	(XC hex)	H
(DP)	X	X	X	X	1	1	0	1	(XD hex)	L
(DP)	X	X	X	X	1	1	1	0	(XE hex)	P
(DP)	X	X	X	X	1	1	1	1	(XF hex)	(blank)

 

Above is the layout of the module without the 7-segment display and below in Fig.4 is the matching circuit diagram.

Fig.3 (left): when 'Code B' decoding is active for a segment, the lower four bits of the value for that segment form a look-up table for one of 16 possible 7-segment display configurations, as shown at right. The top bit determines whether the decimal point is lit. Compare this to (B) at bottom, where decoding is not active and the eight bits in SRAM control the segment drivers directly.


B WHEN DATA BIT 'NO-DECODE' MODE IS SELECTED

DATA BITS								
DP	D7	D6	D5	D4	D3	D2	D1	D0
(DP)	A	B	C	D	E	F	G	

CORRESPONDING SEGMENTS WITH NO DECODING

NOTE: DECODE/NO-DECODE MODE CAN BE SELECTED INDEPENDENTLY FOR EACH OF THE EIGHT DIGITS, USING THE DECODE REGISTER

Fig.4 (below): the circuit of a typical pre-built 8x8 LED matrix module with MAX7219 driver. A photo of this type of module is shown above. There's virtually nothing to it, just the LED matrix display module, the MAX7219 IC and some connectors to join them together and to provide connections to the microcontroller and optionally, more daisy-chained LED displays.

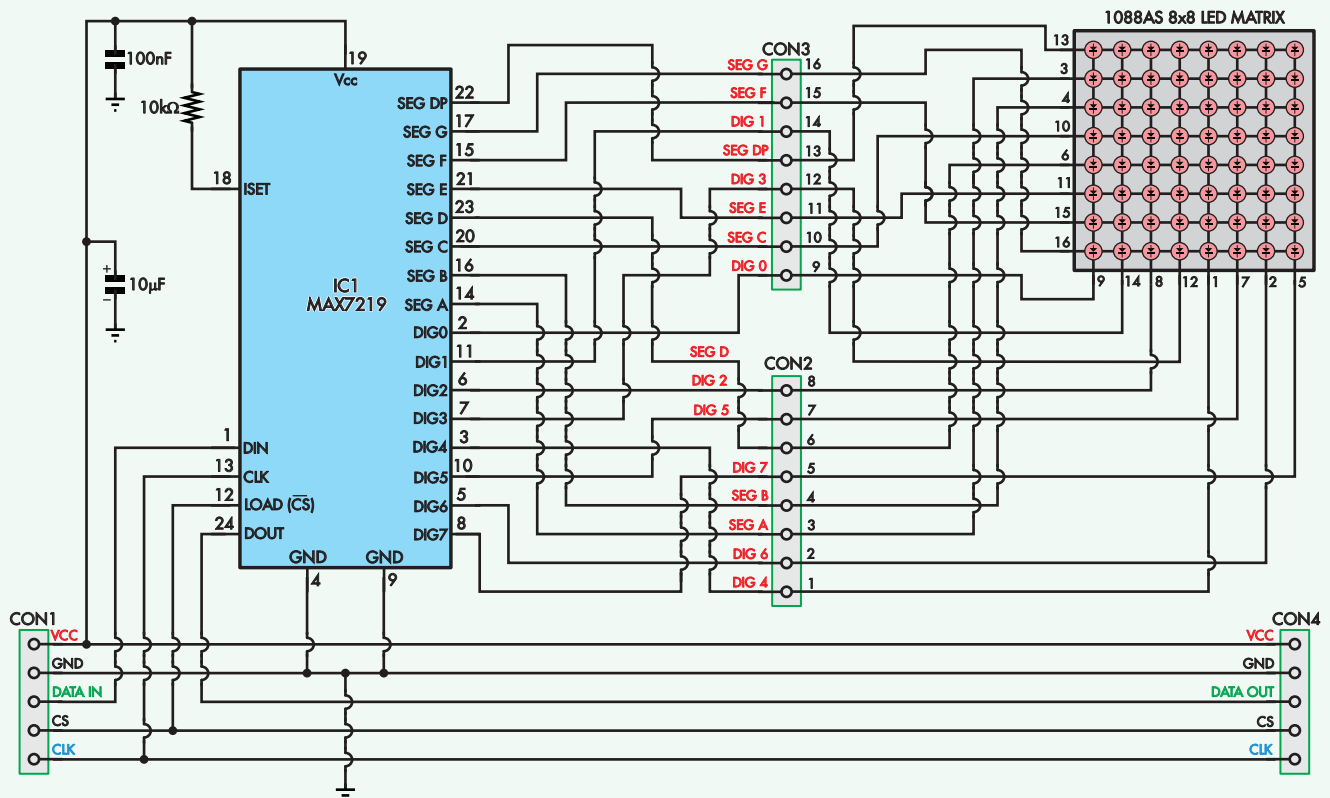


to be connected to the IO10/SS pin of an Arduino Uno, Freetronics Eleven or Duinotech Classic, as shown in Fig.6. With other variants, you should be able to find the corresponding

pin without too much trouble – and even if you can't find it, the pin reference can be changed in your software sketch to match the pin which you decide to use.

Driving them from a Micromite

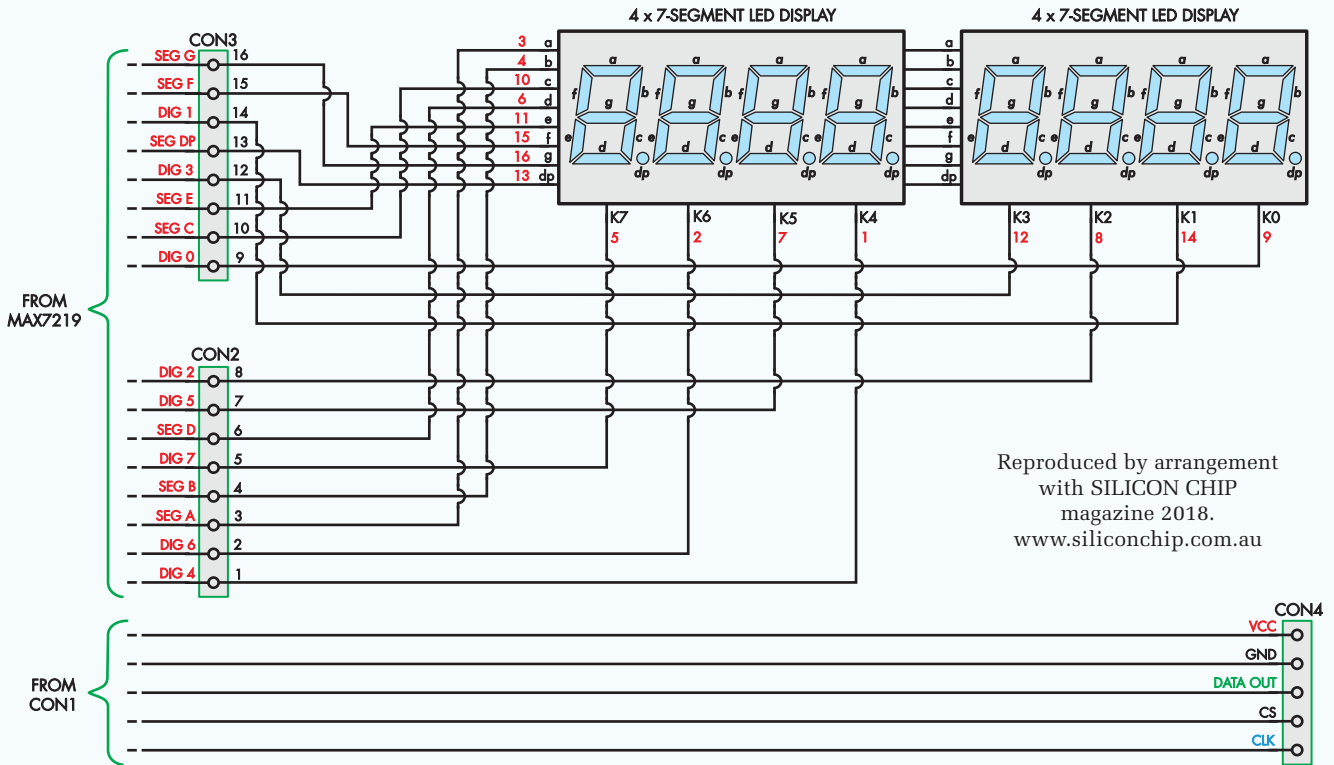It's also quite easy to drive these modules from a Micromite, using the connections shown in Fig.7. By connecting the MOSI, SCK and SS/



Reproduced by arrangement with SILICON CHIP magazine 2018. www.siliconchip.com.au

Fig.5: the circuit of a typical pre-built 8-digit 7-segment common-cathode LED display using a MAX7219. Pre-built modules for this configuration are also available. We haven't shown the IC itself, as its configuration is identical to that of Fig.4 – all that's changed is that in place of the 8x8 LED matrix are two 4-digit 7-segment displays with the anodes wired in parallel.

LOAD lines to Micromite pins 3, 25 and 22 as shown, MMBasic's built-in SPI protocol commands will have no trouble in communicating with the module.

So that's the basic story regarding the hardware side of the MAX7219-based module which can drive either an 8x8 LED matrix array or eight 7-segment LED displays.

Before we finish, a few words are in order regarding the software side, ie, how to write programs to get the module to display what you want.

Writing the software

The basic idea here is that when your program starts up, it needs to carry out a number of set-up tasks:


- Declare the micro's pins that are going to be used by the SPI interface and set them to their idle state (normally high).
- Start up the SPI interface, with its settings configured for a clock rate of say 5MHz, the data to be sent MSB (most-significant bit) first and using clock/data timing mode 0. If possible, it should also be set for

the data to be exchanged in 16-bit words rather than bytes.

- Send the initialisation commands to the MAX7219 to set up its five control registers: shutdown, decode mode, intensity, scan limit and display test.

After these tasks have been done, you should be able to send out the actual display data for each of the 8-digit display addresses in the MAX7219's SRAM. And if the display is to be a dynamic one, you

Fig.6: connecting either type of MAX7219-based module to an Arduino is easy. Simply wire up the SPI pins and power supply to the ICSP header on the Arduino and the CS pin to a free GPIO – ideally IO10, which is the hardware slave select (SS) pin.

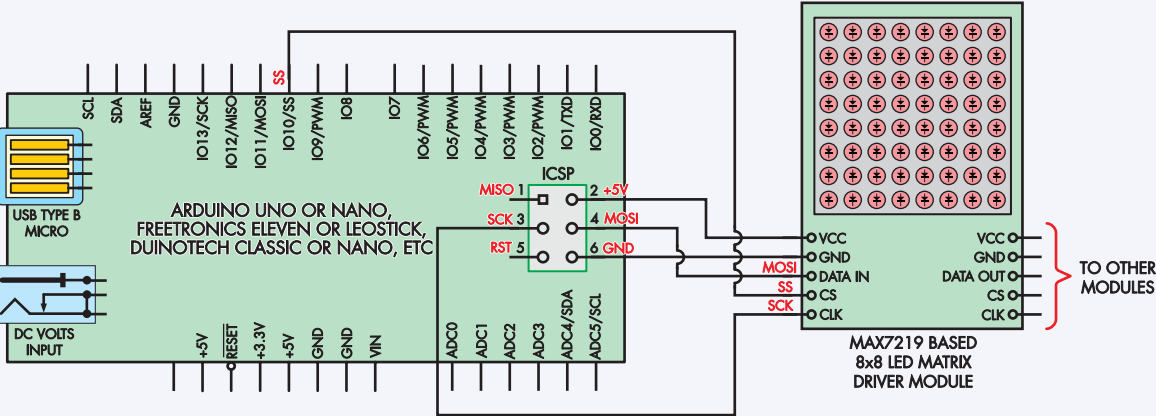

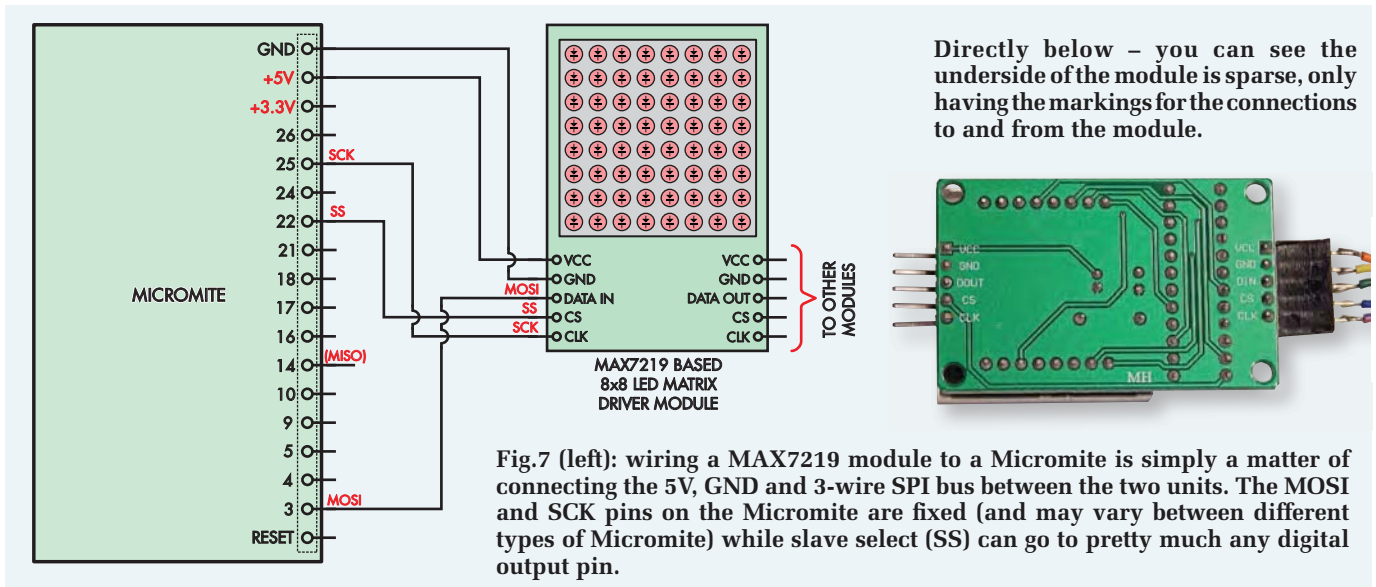


Fig.7 (left): wiring a MAX7219 module to a Micromite is simply a matter of connecting the 5V, GND and 3-wire SPI bus between the two units. The MOSI and SCK pins on the Micromite are fixed (and may vary between different types of Micromite) while slave select (SS) can go to pretty much any digital output pin.

can send out revised data at the appropriate times.

To help you understand what's involved in writing your own programs for the module, I have written a couple of simple example programs which repeatedly display an expanding star pattern on the 8x8 LED matrix array (you can see the fully expanded star on the lead photo).

One of these programs is written for Arduino and I have called it: `sketch2_`

`for_Testing_MAX7219.ino`. The other program is written for the Micromite, and is called `MAX7219 LED array Star.bas` Both of these programs are available for download from the *EPE* website.

Both programs simply blank the display for a second or so, then cause a small square pattern to appear first in the centre of the array and then expand out fairly quickly to form a star, with its tips at the four corners of

the array. The expanded star remains visible for about three seconds before the array is blanked again and the sequence repeats.

It's all quite simple, but either program should give you a reasonably clear guide regarding how to use the MAX7219 display driver module in your own projects.

I've tried to provide a lot of explanatory comments in both programs, to help in this regard.

Tag-Connect

JTAG Connector Plugs Directly into PCB!!
No Header! No Brainer!

Our patented range of Plug-of-Nails™ spring-pin cables plug directly into a tiny footprint of pads and locating holes in your PCB, eliminating the need for a mating header. Save Cost & Space on Every PCB!!

Solutions for: PIC . dsPIC . ARM . MSP430 . Atmel . Generic JTAG . Altera Xilinx . BDM . C2000 . SPY-BI-WIRE . SPI / IIC . Altium Mini-HDMI . & More

www.PlugOfNails.com

Tag-Connector footprints as small as 0.02 sq. inch (0.13 sq cm)

Electronics & Robotics for Makers

ICSAT's *Pixie* system for Education and Hobbyists now adds ATtiny based mainboards to the PICAXE and Genie based versions.

Pixie 8 & 14 mainboards, simple standalone boards that provides one or two standard *Pixie* port connectors for power and I/O connections. PICAXE and Genie versions have the 3.5mm download socket and the ATtiny versions have the ATMEL 6 pin ICSP programming connector.

Pixie ATtiny programmers, we have two versions. One that is a mini shield for the Arduino Uno complete with 6 pin ICSP connector. The second one is a complete unit based upon the Arduino Nano, which is pre-programmed and ready to go, you just need to update your Arduino IDE, with the ATtiny board information.

Pixie Sprite is a complete module with I/O connections and 2 bidirectional motor outputs powered by an L293D, and is available in all 3 chip types: PICAXE, Genie and Attiny84. The board can use crocodile clips and 1 pin headers for use with jumpers - a great solution for education and Robotics.

The *Pixie 8* and 14 pin mainboards have one or two *Pixie* ports which provides power and I/O connections, all our *Pixie Dot* and *Pixie Hot* project boards are fully compatible with them.


Supporting Education
Supporting Makers

www.eshop.icsat.co.uk



MAX7218 8x8 Dot Matrix Display Module

This is 8x8 (row by column 64x LED) dot matrix LED displays module based on MAX7219 IC. The displays are designed so that they can be mounted in a horizontal chain and can also be expanded in a vertical plane allowing versatile displays panel to be built. A convenient 3-wire serial interface connects to all common controller board like Arduino or Raspberry. Individual dot may be addressed and updated without rewriting the entire display. This module can be daisy chain to form a display panel for scrolling message board.

 

SKU: [DSP-1172](#)


Brief Data:

- Matrix Size: 8x8 (64-Dots)
- Display Size: 1.3”.
- Display Color: Red.
- Interface: 3-Wires Serial Interface.
- Daisy chain for multiple modules.
- Operating voltage: 4.5 ~ 5V.
- Module size: 5 x 3.2 x 1.5cm (L x W x H).
- Mounting Hole: M3.



MAX7219 32x8 Dot Matrix Display Module

This is 8x8 (row by column 64x LED) dot matrix LED displays module based on MAX7219 IC. The displays are designed so that they can be mounted in a horizontal chain and can also be expanded in a vertical plane allowing versatile displays panel to be built. A convenient 3-wire serial interface connects to all common controller board like Arduino or Raspberry. Individual dot may be addressed and updated without rewriting the entire display. This module can be daisy chain to form a display panel for scrolling message board.

 


SKU: [DSP-1172](#)

Brief Data:

- Matrix Size: 32x8 (256-Dots)
- Display Size: 128x33 mm.
- Display Color: Red.
- Interface: 3-Wires Serial Interface.
- Daisy chain for multiple modules.
- Operating voltage: 4.5 ~ 5V.
- Module size: 128 x 33 x 15 mm (L x W x H).
- Mounting Hole: M3.

Li-Ion and LiPo Charger Modules

 

These modules are designed to charge Lithium-ion and Lithium-ion polymer cells. One is low-cost and has a simple design, while the other sports an inbuilt DC-DC boost converter to provide a regulated output voltage from the Li-ion/LiPo cell, since its voltage varies as it charges and discharges.

Using Cheap Asian Electronic Modules Part 8: by Jim Rowe

Lithium-ion (Li-ion) and lithium-ion polymer (LiPo) cells and batteries are rapidly overtaking all earlier kinds of rechargeable energy storage. They're now being used in just about all mobile and cordless phones, in USB Power Bank devices used to recharge them, in laptop and tablet PCs and in many portable power tools.

Not only that, but it now looks like Li-ion/LiPo batteries are the preferred power source in the most successful current generation of electric cars, as well as providing some small-scale grid storage.

So it's not surprising that Li-ion/LiPo charging modules have now become readily available on popular internet venues like eBay and AliExpress, and we will be looking at three examples in this article.

Basic charger modules

Probably the most common charger modules you'll find on the web are those based on the TP4056 charge controller chip, like the one shown opposite in the photo at lower right. These modules are quite tiny, measuring only 26 × 20mm and they're currently available for just a few pounds each, even in small quantities.

There are a few minor variations, but most are very similar to the one pictured; and they are all slight variations of the circuit shown in Fig.1. Some are fitted with a micro-USB type B socket on the input side, while others have the slightly larger and more rugged mini-USB type B socket. You might choose this type since micro-B sockets can be a bit fragile and can even part from the module PCB when you're removing the USB cable.

Having said that, micro-B cables are very common and cheap because they are used to charge most modern smartphones, so that's a fairly strong reason to prefer the micro version, even if it's a bit more fragile.

As shown in Fig.1, there's little in one of these modules apart from the TP4056 controller chip itself. Made by Chinese firm Nanjing Top Power ASIC Corp, the TP4056 comes in a compact SOIC-8 package and provides all of the functions of a single-cell Li-ion/LiPo battery charger, powered from a 5V USB-compatible supply.

It follows the standard CC-CV charging protocol, with a maximum current of 1000mA (1A) in CC (constant current) mode and a maximum voltage of 4.2V (±1.5%) in CV (constant voltage) mode. Charging is automatically terminated when the charge current falls to 10% of the programmed value.

The charging current in CC mode can be programmed by changing the value of the R_{PROG} resistor connected between pin 2 of the IC and ground. As supplied, the module has a 1.2k Ω resistor fitted, corresponding to a charging current of 1000mA. If you want a lower charging current, you can select a higher value resistor – as shown by the table at upper right in the diagram.

For example, if you replace the resistor with one of 2.0k Ω , the charging current in CC mode will drop to around 580mA. However, that should only be necessary if the cell you're charging has a capacity of less than 1Ah, which would make it quite small, and even some cells under 1Ah would be OK being charged at 1A; if in doubt, check the manufacturer's ratings for that cell.

As well as performing all of the charge control functions, the TP4056 also controls two indicator LEDs to signal the charger's current state. Red LED1 glows brightly during both charging modes (CC and CV) and ceases glowing when charging is terminated. Green LED2 only lights when charging is terminated. Both LEDs remain off if the USB input voltage is too low (<4.0V) or there is no cell or battery connected.

Note that if you want to power the charger from the USB port of your PC or laptop, it would be a good idea to change the value of R_{PROG} to 2.4k Ω so that the charging current is reduced to around 500mA; this is the maximum that should be drawn from the USB port of a PC (even though many ports will allow you to draw 1A if you try, at least for a short period). But if you are powering the charger from one of the 5V/1A USB plug packs, R_{PROG} can be left at its default value of 1.2k Ω .

That's about it for the basic versions of the USB-powered Li-ion/LiPo charger. They're cheap as chips but they actually do quite a good job of charging single cells and parallel-cell batteries.

Do keep in mind though that the TP4056 is a linear device, utilising an internal P-channel MOSFET to reduce the incoming supply voltage of say 5.5V down to the charging voltage of the cell, which could be as low as 3V when fully discharged. At a 1A charge current, that's a dissipation of (5.5V – 3V) × 1A = 2.5W which is quite substantial for an SOIC-8 package and it's likely to get quite hot under this condition (even more so if you run the chip at its maximum input supply rating of 8V).

This won't cook the chip since it has thermal regulation, which essentially means that it reduces the charging current if it gets too hot. But it does mean that it will take longer to charge the cell if you run into thermal limiting and the charging process won't be terribly efficient. Considering the size and cost of these modules, that really isn't a problem.

Fancier versions

In addition to the basic charger modules, there are more elaborate versions available. One of the most popular of these is shown on the next page. It's made by the firm Elecrow, based in Shenzhen, China, and is about four times the size of the basic modules, measuring 68 × 49mm.


The circuit is shown in Fig.2. The actual Li-ion charger section is based around IC2 at the top. This is a Consonance CN3065 chip, which functions in much the same way as the TP4056 device used in the basic modules. As before, the CC mode current level is set via the resistor R_{PROG} connected between pin 2 (I_{SET}) and ground, and the default value of 2.0k Ω for this resistor gives a charging current of 900mA.

The CN3065 again follows the standard CC-CV protocol, with mode switching at 4.2V \pm 1% and charging terminated when the current in CV mode drops to 10% of the programmed CC level. An interesting extra feature is that the cell voltage level at which the device switches from CC mode to CV mode can be raised above 4.2V by adding an external resistor between pin 5 (BAT) and pin 8 (FB). This will result in it reaching full charge sooner.

As with the TP4056, the CN3065 provides outputs to drive two LEDs. LED1 lights during charging, while LED2 lights when charging has terminated. Incidentally, the CN3065 is in a very tiny (3 × 3mm) DFN-8 leadless SMD package.

Another nice feature of the Elecrow PSB01012B charger is that it provides a choice of two DC inputs. One is via CON2, the mini-USB input socket, while the other is via CON1, a JST 2.0mm socket designated as the input from a solar photovoltaic panel. (A second JST 2.0 socket [CON3] is used for the Li-ion cell connection.) Schottky diodes D1 and D2 are used to feed the two inputs to IC2, so no input switching is required.

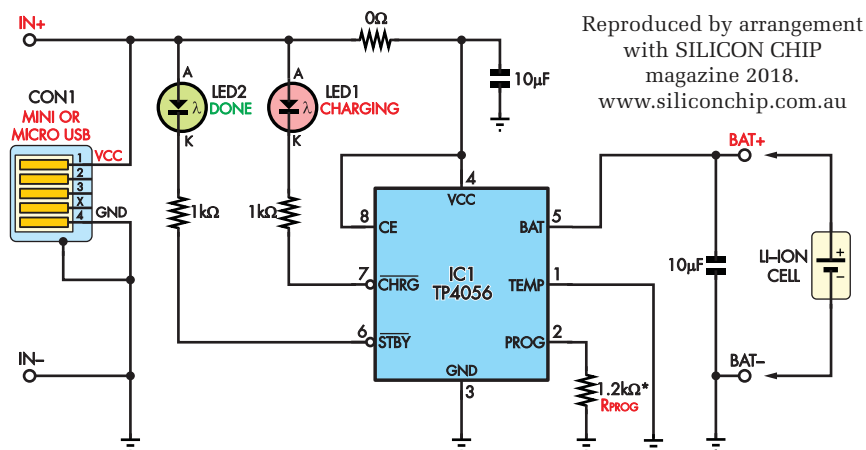Note that the D- and D+ USB data lines of CON2 are taken through to USB output socket CON4, a standard USB type A socket. That's because the PSB01012B is not just a charger, but in effect a USB Li-ion power pack as well. It's also the reason for on-off



Reproduced by arrangement with SILICON CHIP magazine 2018. www.siliconchip.com.au

*DEFAULT VALUE. SEE TABLE AT RIGHT TO REDUCE CHARGING CURRENT

CHANGING THE CELL CHARGING CURRENT BY ALTERING THE VALUE OF R _{PROG}								
R _{PROG} value:	1.2k Ω	1.3k Ω	1.5k Ω	1.8k Ω	2.4k Ω	3.3k Ω	4.7k Ω	12k Ω
I _{BAT} in mA:	1000	923	800	667	500	363	255	100

Fig.1: circuit diagram for the basic TP4056 module. Note that many modules of this type will differ slightly from this circuit diagram.

switch S1, in series with battery connector CON3. But note that S1 will need to be in the ON position for charging to take place.

The other half of the Elecrow PSB01012B module provides a regulated +5V supply from the varying output of the Li-ion cell. This is the function of the circuitry around IC1, REG1 and IC3, in the lower half of Fig.2.

IC1 is the actual output voltage regulator. This is an Intersil ISL97516 device, described as a high-frequency, high-efficiency step-up (boost) voltage regulator, which operates in a constant frequency PWM mode. It's in a very small MSOP-8 package.

The ISL97516 operates at a nominal frequency of 620kHz or 1250kHz, selected by connecting pin 7 (F_{SEL}) to ground or pin 6 (V_{DD}). As you can see from Fig.2, in the Elecrow module it's programmed for 620kHz. The switching FET inside the device has a maximum current limit of 2.0A and an on-resistance of 200m Ω . As a result, it's claimed to deliver over 90% conversion efficiency – quite impressive.

The input voltage range of the ISL97516 is rated at 2.3-5.5V, which is well suited to its application here. The output voltage range is specified as 5-25V. The actual output voltage is determined by the proportion of the output voltage fed back to pin 2 (FB) of the device, via a resistive divider. In the Elecrow module, the divider formed from the 43k Ω and 15k Ω resistors programs it to give an output of 5V.


Other attractive features of the ISL97516 include sensing of the current in the switching FET for thermal overload protection and a soft-start feature which allows slowing down of the internal oscillator's startup by connecting a capacitor from pin 8 (SS) and ground. As you can see in the

Elecrow module, a 27nF capacitor is used for this.

The regulated 5V output from IC1 appears across the 47 μ F capacitor at the cathode of diode D3 and is then filtered before being fed to pin 1 of the USB output connector CON4.

So that's the boost converter/regulator section. But what about the rest of the module's circuit, involving REG1 and two op amps in IC3? This additional circuitry is basically to monitor the Li-ion/LiPo cell voltage, and signal if it drops below a safe level. REG1 is a Micrel MIC5205-2.5 low noise LDO regulator, used to derive a 2.5V \pm 1% reference from the cell voltage.

 This is fed to op amps IC3a and IC3b, which are used as comparators. The second input of each 'comparator' is fed with a proportion (0.6875) of the cell voltage, derived by the resistive divider formed by the 150k Ω and 330k Ω resistors.



This TP4056 module shown uses a micro-USB^[2] connector, but there are some that use mini-USB^[1].

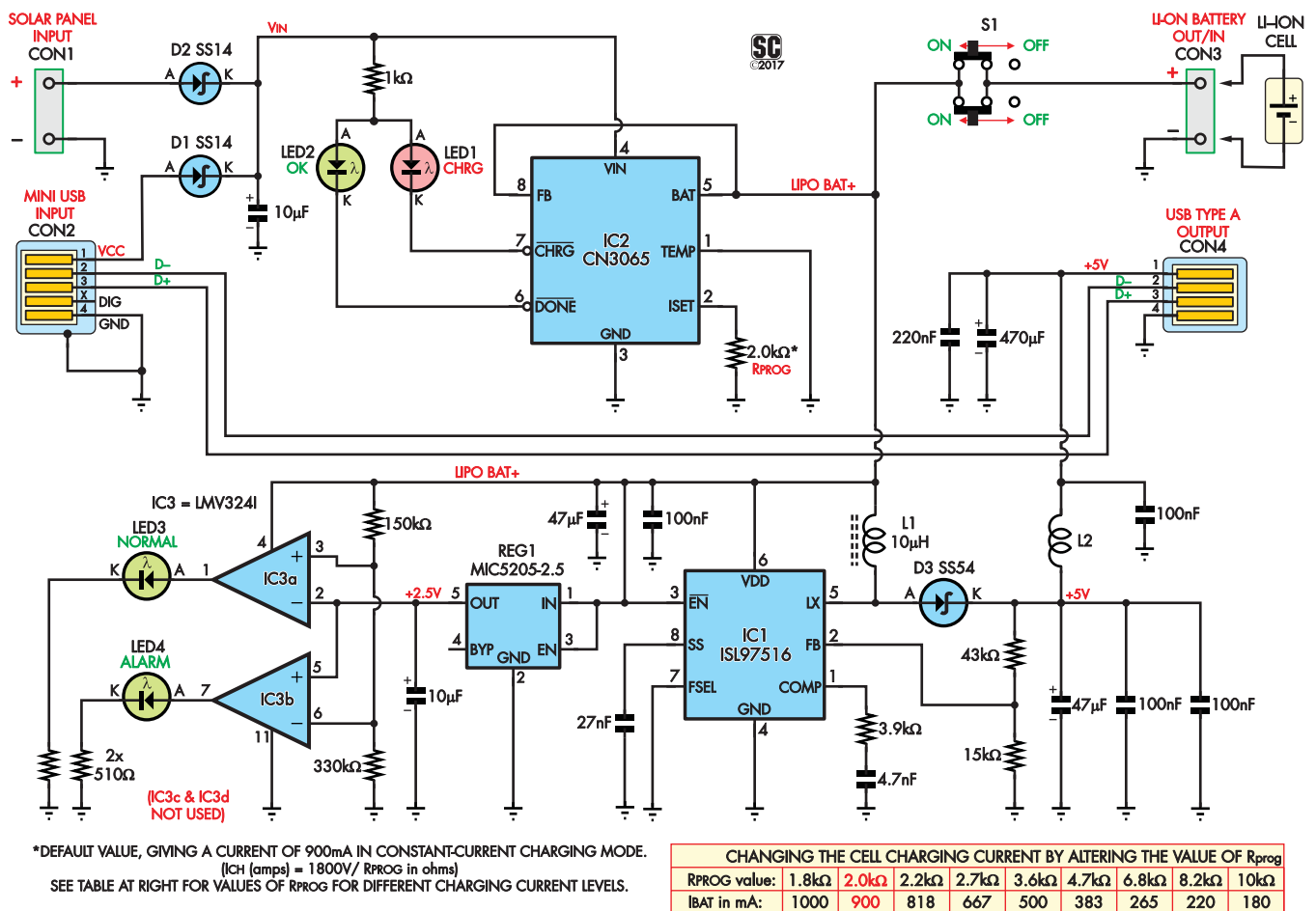


Fig.2: circuit diagram for the Elecrow PSB01012B charger module which utilises a CN3065 IC instead of the TP4056 detailed earlier (the CN3065 is functionally identical to the TP4056).

This voltage is fed to the positive input of the IC3a comparator and the negative input of the IC3b comparator. As a result, whenever the divided-down cell voltage is above +2.5V, IC3a turns on LED3 to indicate that the cell voltage is OK.

By contrast, if the divided-down cell voltage falls below +2.5V, IC3a turns off LED3 and IC3b turns on LED4 to indicate that the cell is nearing the limit of safe discharging. This occurs at $2.5V \div 0.6875 = 3.64V$, a little above the minimum recommended discharge voltage to achieve the best cell lifespan.

So the Elecrow charger module with its inbuilt +5V output regulator provides significantly more capabilities than the basic modules. It actually provides all of the functions needed for making your own USB Power Bank, using a Li-ion or LiPo cell/battery of your own choosing. Plus, it has the ability to charge your Li-ion/LiPo cell from a solar panel.

So although it will cost you significantly more than one of the basic modules, it's still good value for money.

Trying them out

I tried a couple of the basic TP4056-based charger modules with both a single 18650 Li-ion cell and a battery of two parallel-connected 18650 cells.

The chargers did everything that could be expected from them, charging the cells repeatedly with no problems – apart from the micro-B USB input socket breaking away from one of the modules when I tried to unplug the cable from the USB plug pack. Hence my suggestion to prefer the mini-USB socket version.

I also tried out one of the fancier Elecrow PSB01012B modules, although this did involve getting hold of some cables with the very small JST 2.0 connectors (for the Li-ion cell cables, to connect to CON3).

As a charger, this one worked just as well as the basic modules. But where it really shone was on the output side, being able to provide a regulated +5V output (or reasonably close to it; about 4.85V) for the USB device connected to CON4's output, even for a load drawing 500mA and with a partly discharged Li-ion cell with a terminal voltage down to about 3.8V.

In fact, it kept providing this regulated output voltage even when the Li-ion cell dropped down below 3.0V, after about 40 minutes. Quite impressive! (But not recommended if you want your cell to last a long time.)

It might seem to be nit-picking, but I'd like to have seen the Elecrow module's regulated USB output closer


to the nominal +5V under load than 4.85V. If you calculate the expected output voltage for IC1, you get $1.294V \times (43k\Omega \div 15k\Omega + 1) = 5.0V$, so this is likely a component tolerance issue that requires trimming.

This could be achieved by measuring the actual output voltage and then paralleling the 15kΩ resistor with a higher value SMD resistor, by soldering it on top. For example, in my case, the output needs to be raised by $(5.0V - 4.85V) \div 4.85V = 3.1\%$, so a resistor of $15k\Omega \div 0.031 = 483,870\Omega$ or say 470kΩ should do the trick.

I also think that ALARM LED4 should ideally be a red one, not another green one as it is at present. It's right next to green LED3, making it difficult to see when LED4 has lit up. You could fix this by de-soldering LED4 and fitting a red LED in its place.

My only other complaint about the Elecrow module was that the very small slider switch used for power switch S1 was very flimsy. Perhaps it had been damaged in transit, but at one point the tiny actuator almost came out of the switch body – not a good sign.

 One more point – it would be a good idea if the unit could be set up to automatically switch off the output if the cell voltage drops too low, to prevent damage from over-discharge. Some



The Elecrow charger module is a more advanced version of the smaller module, and provides a 5V regulated supply from the Li-ion cell.^[3]

Li-ion and LiPo cells have internal over-discharge protection circuitry, but many do not. It would be possible to modify the module to provide this function, by cutting the track to pin 3 of IC1 and soldering it to output pin 1 of IC3a instead.

However, note that this would cut off the output at the aforementioned cell voltage of 3.64V, which is a little high; ideally, alarm LED4 should light before the cell is discharged to the point where the output switches off. A second threshold in the range of 3.0-3.3V would do the trick, but that would require a number of extra components.


Smaller Elecrow module

It was only after I had checked out the Elecrow PSB01012B module that I learned about their other ‘mini’ module. Luckily I was able to get a hold of one of these quickly, in order check it out as well.

As you’d expect from the circuit (Fig.3), its performance as a Li-ion cell charger is very close to that of its bigger brother – it just takes a little longer to charge, because of the lower default charging current level.

It functions in a very similar manner but is significantly smaller (46 × 32mm), costs less and they have made some tweaks to the design. It uses the same CN3065 chip for charging as the larger module. However, unlike the larger module, it does not have

 There isn’t much going on underneath the Elecrow module, except for a few tracks and the eight through-hole pads provided for D+ and D- biasing resistors.^[3]



a power switch, so the load is always powered.

I was interested in measuring the performance of its DC-DC boost converter, because of its greater simplicity. And I was pleasantly surprised, because the converter in the mini module was just as good as the one in its big brother.

Even though its output voltage under 250mA of loading was slightly lower at 4.80V with a cell voltage of 3.84V, it only dropped to 4.78V when the cell voltage fell to the recommended minimum of 3.0V. So it might be a lot simpler, but it’s just as impressive in terms of conversion efficiency.

The other differences are as follows. First, the input power socket is a micro type-B, rather than mini. Second, the output current capability is lower, at 500mA compared to 1A.

They have also added a JST 2.0 2-pin output connector in parallel with the USB output, and added a pass-through function, which feeds the input voltage directly through to the output when it is present, to reduce the load on the cell.

There are a couple of drawbacks to this module, though. Note that the USB and solar inputs are wired in parallel, so there’s a possibility of current

being fed back into the USB source, which would be bad. Also, if the USB supply voltage is high enough, Q1’s body diode could allow current to pass into the cell, bypassing IC1 and possibly leading to over-charging.

This is likely a design oversight and will probably be fixed in future revisions, but could be solved by placing a diode in series with Q1; a notable omission from the design.

The bottom line

Overall then, all of these modules seem to work quite well. The basic charger modules are fine if you just want to charge a Li-ion/LiPo cell (or two in parallel), although I would recommend the version with a mini-B USB input socket rather than a micro-B socket, for the greater robustness.


With the enhanced Elecrow PSB01012B and mini variant, the main reason to go for the larger PSB01012B module is for its ‘through path’ for the USB signal lines between the input and output, and for its use of the more reliable mini-B USB input connector.

One final note: if you want to use either a basic charger module or one of the fancier modules to charge one of the flat pack LiPo cells, then you’ll probably need to get a matching charging cradle to make reliable connections to the contacts on the end of the cell. These cradles are available at quite a low price from sites like eBay or AliExpress, although some of them come with their own inbuilt chargers.


Finding the charging modules

All of these chargers are available on the Internet; here are some tips:

 - 1) TP4056 1A Li-ion/LiPo charger with mini-USB socket is available from eBay.co.uk – for example, item 222179387315.
- 2) TP4056 1A Li-ion/LiPo charger with micro-USB socket is available from eBay.co.uk – for example, item 332563978016.
- 3) Elecrow CN3065-based 1A Li-ion/LiPo charger with 1A step-up circuit, USB pass-through and power switch;



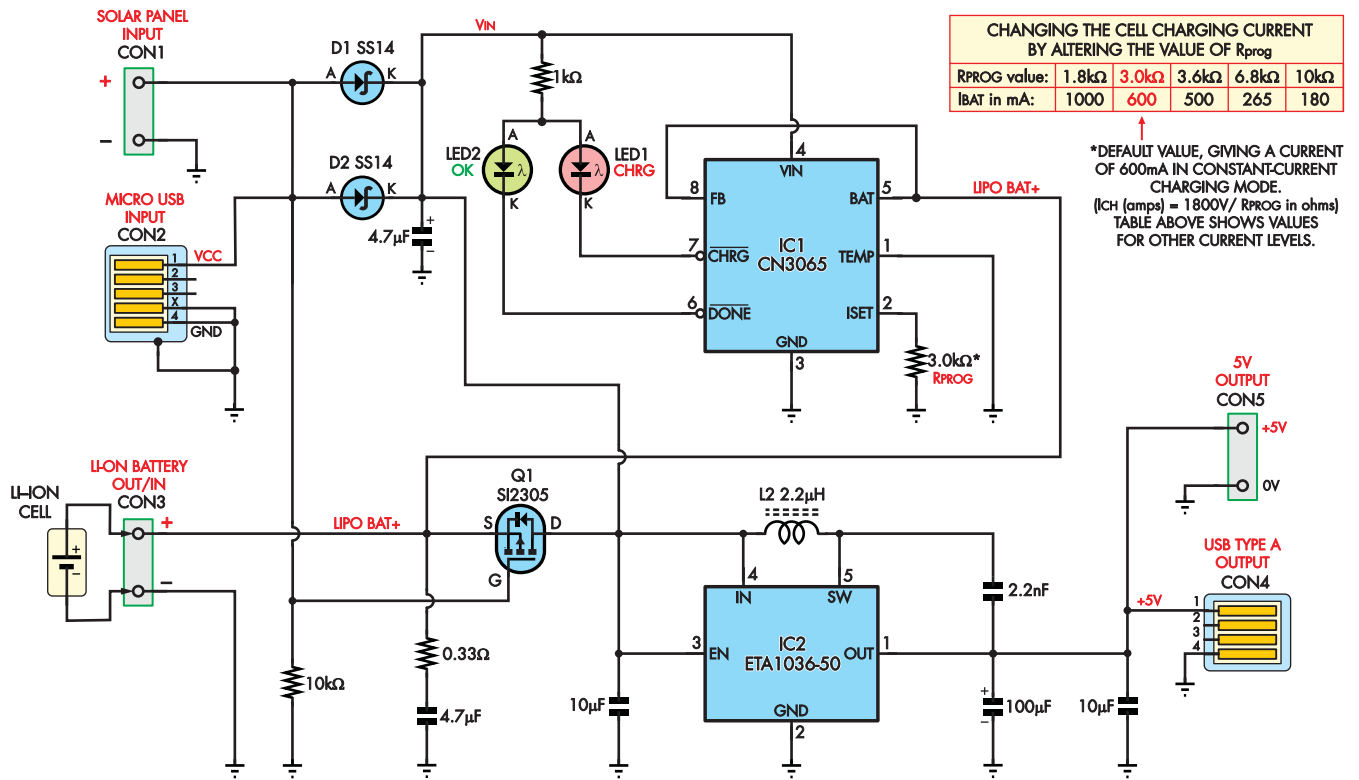The mini Elecrow module is a decent bit smaller (46 × 32mm) than the larger variant (68 × 49mm).^[4]



CHANGING THE CELL CHARGING CURRENT BY ALTERING THE VALUE OF R _{prog}				
R _{prog} value:	1.8kΩ	3.0kΩ	3.6kΩ	10kΩ
I _{BAT} in mA:	1000	600	500	265

*DEFAULT VALUE, GIVING A CURRENT OF 600mA IN CONSTANT-CURRENT CHARGING MODE.
(I_{CH} (amps) = 1800V/ R_{prog} in ohms)
TABLE ABOVE SHOWS VALUES FOR OTHER CURRENT LEVELS.

Fig.3: circuit diagram for the smaller Elecrow charger module. The DC-DC boost converter is much simpler than the larger Elecrow module and is based around an ETA1036-50 synchronous converter chip (IC2; SOT23-5). This allows for a drastic simplification of the boost converter to a 2.2µH inductor, four SMD capacitors plus the IC. Q1 allows the incoming 5V from USB or a solar cell to power IC2 directly, bypassing the cell.

68 × 49mm, mini type-B USB input, full-size type-A USB output, two JST cables included is available from elecrow.com – item PSB01012B.

4) Elecrow CN3065-based 1A Li-ion/LiPo charger with 500mA step-up circuit; 46 × 32mm, micro type-B USB input, full-size type-A USB

output, three JST cables included is available from elecrow.com – item CPC09141S.

FANTASTIC MODERN POWER SUPPLY ONLY IU HIGH PROGRAMMABLE			
AM AGE ES S PSU GE 100 1 100 1 A o ed As e			32
AM AGE ES S PSU GE 0 30 0 30A			32
202	Si nal Gene ato 9 2. 1G pt 04/11		900
Ma con 29	adio o unications Test Set		800
&S AP 62	S n unction Gene ato 1 260K		19
P332 A	S nthesised unction Gene ato		19
P3 61A	na ic Si nal Anal se		6 0
P6032A	PSU 0 60 0 0A 1000		0
P6622A	PSU 0 20 4AT ice o 0 2AT ice		3 0
P6624A	PSU 4 utputs		3 0
P6632	PSU 0 20 0 A		19
P6644A	PSU 0 60 3. A		400
P66 4A	PSU 0 60 0 9A		00
P8341A	S nthesised S eep Gene ato 10M 20G		2 000
P83 31A	S nthesised Si nal Gene ato 1 20G		1 800
P8484A	Po e Senso 0.01 18G 3n 10u		
P8 60A	Spect u Anal se S nthesised 0 2.9G		1 2 0
P8 60E	Spect u Anal se S nthesised 30 2.9G		1 0
P8 63A	Spect u Anal se S nthesised 9K 22G		2 2 0
P8 66	Spect u Anals e 100 22G		1 200
P8662A	Gene ato 10K 1280M		0
Ma con 2022E	S nthesised AM/ M Si nal Gene ato 10K 1.01G		32
Ma con 2024	S nthesised Si nal Gene ato 9K 2.4G		800
Ma con 2030	S nthesised Si nal Gene ato 10K 1.3 G		0
Ma con 230	Modulation Mete		2 0
Ma con 2440	ounte 20G		29
Ma con 294 /A/	o unications Test Set aious ptions		2 000 – 3 0
Ma con 29	adio o unications Test Set		9
Ma con 29 A	adio o unications Test Set		2
Ma con 6200	Mic o a e Test Set		1 00
Ma con 6200A	Mic o a e Test Set 10M 20G		1 9 0
Ma con 6200	Mic o a e Test Set		2 300
Ma con 6960	ith 6910 Po e Mete		29

Te t oni T S30 2 /	scilloscope 00M 2. GS/S	1 00
Te t oni T S3032	scilloscope 300M 2. GS/S	99
Te t oni T S3012	scilloscope 2 hannel 100M 1.2 GS/S	4 0
Te t oni 2430A	scilloscope ual T ace 1 0M 100MS/S	3 0
Te t oni 246	scilloscope 4 hannel 400M	600
a nell AP60/ 0	PSU 0 60 0 0A 1K S itch Mode	19
a nell 60/ 0	PSU 0 60 0 0A	00
a nell A3 /2T	PSU 0 3 0 2AT ice i ital	
a nell 1	Sine/s scillato 10 1M	4
acal 1991	ounte /Ti e 160M 9 i it	1 0
acal 2101	ounte 20G E	29
acal 9300	T ue MS Milli olt ete 20M etc	4
acal 9300	As 9300	
lu e 9	Scope ete 2 hannel 0M 2 MS/S	
lu e 99	Scope ete 2 hannel 100M GS/S	12
Gi at onics 100	S nthesised Si nal Gene ato 10M 20G	1 9 0
Sea a d o a	PAT Teste	9
Sola ton 1 0/P US	6 1/2 i it MM T ue MS EEE	6 /
Solat on 12 3	Gain Phase Anal se 1 20K	600
Tasa a o TM03 2	PSU 0 3 0 2A 2 Mete s	30
Thu l P 320 M	PSU 0 30 0 2AT ice	160 200
Thu l TG210	unction Gene ato 0.002 2M TT etc Ken ood ad ed	6
P33120A	unction Gene ato 100 ic o 1 M	260 300
P 3131A	Uni e sal ounte 3G o ed unused	00
P 3131A	Uni e sal ounte 22 M	3 0

UST STA A MM	ES A P 100M S PE
32 2 T UT A E	A MP ETE T A
A UMPE S	A ESS ES 12
HP 34401A Digital Multimeter 6 1/2 Digit	HP 54600B Oscilloscope Analogue/Digital Dual Trace 100MHZ

MARCONI 2955B Radio Communications Test Set 800	P PE 200M A A GUES PE 2 0
A ESUPP E T PT A T A ST ASE	FLUKE/PHILIPS PM3092 Oscilloscope 2+2 Channel 200MHZ Delay TB, Autoset etc



18650 Lithium Battery Charger Module with Protection

5V microUSB 1-Amp 18650 Lithium Battery Charging Board Charger Module+Protection. This versatile charger module is based on TP4056 IC, a constant-current/constant-voltage linear charger chip for single cell lithium-ion batteries. This charger module can be powered from USB or wall adapter. The features include current monitor, under voltage lockout, automatic recharge and two status LED to indicate charge termination and the presence of an input voltage.



SKU: [MDU-1000](#)


Brief Data:

- High Quality double side PCB design.
- Charge mode - Linear charging.
- Charges Single Cell Li-Ion Batteries Directly from USB Port.
- Charging Current: Preset to 1A max. (with R3=1.2K Ω)
- C/10 Charge Termination.
- Preset 4.2V Charge Voltage with 1.5% Accuracy.
- Input voltage: 4.5V-5.5V.
- Full charge voltage: 4.2V.
- Led indicator- red is charging, blue is full charged.
- Power Input interface: micro USB and terminal pin.
- Work temperature: -10 $^{\circ}$ C to +85 $^{\circ}$ C.
- Built-in protection circuit.
- Size- small to 25x19x1 mm.



3-Cells Lithium Battery Charger with Protection

 This is a protection module for 3-serial-cell lithium-ion / lithium polymer rechargeable batteries and includes a high-accuracy voltage detector and delay circuit. Automatically cancel protection after fault conditions removed. With Protection function of overcharge, over-discharge, short circuit and over-current protection. Suitable for lithium battery pack of 11.1V, 12V & 12.6V.



SKU: [PSU-1012](#)

Brief Data:

- Overcharge Voltage Detection: $3.9\sim 4.35V \pm 0.05V$.
- Over discharge voltage Detection: $2.3\sim 3.0V \pm 0.05V$.
- Maximum operating current: 6~8A.
- Quiescent current: $< 30\mu A$.
- Internal resistance: $< 100m\Omega$.
- Charging voltage: 12.6V ~ 13V.
- Working temperature: $-40\sim +50^{\circ}C$
- Short circuit protection: Yes, delayed self recovery.
- Dimensions: (50 x 16 x 1) mm



Handsontec.com

We have the parts for your ideas

HandsOn Technology provides a multimedia and interactive platform for everyone interested in electronics. From beginner to diehard, from student to lecturer. Information, education, inspiration and entertainment. Analog and digital, practical and theoretical; software and hardware.



open source
hardware

HandsOn Technology support Open Source Hardware (OSHW) Development Platform.

Learn : Design : Share

www.handsontec.com

The Face behind our product quality...

In a world of constant change and continuous technological development, a new or replacement product is never far away – and they all need to be tested.

Many vendors simply import and sell without checks and this cannot be the ultimate interests of anyone, particularly the customer. Every part sell on Handsotec is fully tested. So when buying from Handsontec products range, you can be confident you're getting outstanding quality and value.

We keep adding the new parts so that you can get rolling on your next project.



www.handsontec.com

[Breakout Boards & Modules](#)



[Connectors](#)



www.handsontec.com

[Electro-Mechanical Parts](#)



www.handsontec.com

[Engineering Material](#)



www.handsontec.com

[Mechanical Hardware](#)



[Electronics Components](#)

P



www.handsontec.com

[Power Supply](#)



[Arduino Board & Shield](#)

[Tools & Accessory](#)



www.handsontec.com

[Tools & Accessory](#)